

FACTS


Flexible AC Transmission System

Presented by:
Dr Ahmed Massoud

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

POWER SYSTEM

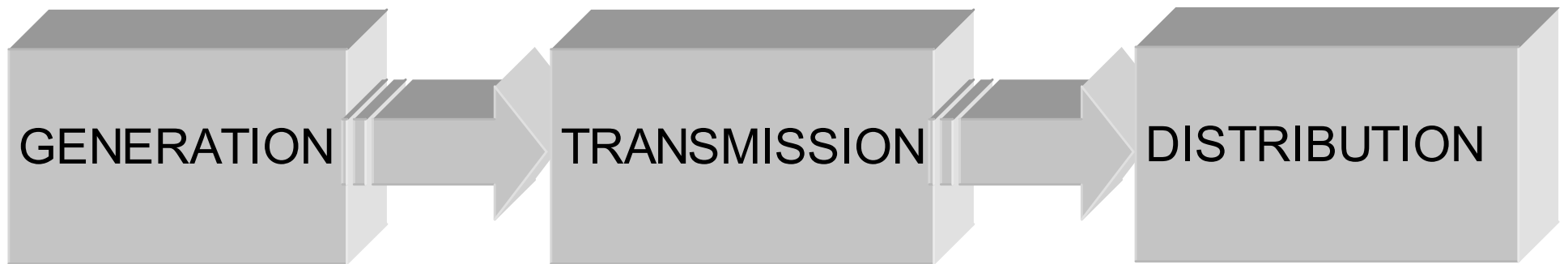

Characteristics of Transmission Bottlenecks

- **Steady-State Power Transfer Limit**
- **Voltage Stability Limit**
- **Transient Stability Limit**
- **Thermal Limit**
- **Short-Circuit Current Limit**

Conventional System Solutions to enhance Transmission capability

- **Series Capacitors (X)**
- **Switched Shunt-Capacitor and Reactor (V)**
- **Transformer LTC's (V)**
- **Phase Shifting Transformers (δ)**
- **Synchronous Condensers (V)**

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

Flexible Alternating Current Transmission Systems (FACTS)

FACTS

AC transmission systems incorporating the power electronic-based to enhance controllability and increase power transfer capability.

FACTS Controllers

A power electronic based system & other static equipment that provide control of one or more AC transmission parameters.

Power Electronics Devices For FACTS Controllers

Line-Commutated

- Thyristors
- Electrically Triggered (ETT)
- Light Triggered (LTT)

Self-Commutated

- Gate-Turn Off Thyristors (GTO)
- Insulated Gate Bipolar Transistors (IGBTs)
- Integrated Gate Commutated Thyristors (IGCTs)

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

FACTS controllers


line commutated

<p>Series thyristor controlled series capacitor (TCSC)</p>	<p>Shunt thyristor controlled reactor or switched capacitor (TCR or TSC)</p>
<p>Back-to-back conventional HVDC</p>	<p>Series-series interline power flow controller (IPFC)</p>



forced commutated

<p>Series static synchronous series compensator (SSSC)</p>	<p>Shunt static synchronous compensator (STATCOM)</p>
<p>Shunt-Series unified power flow controller (UPFC)</p>	<p>Series-series interline power flow controller (IPFC)</p>
<p>Battery energy storage (BESS)</p>	<p>Superconducting Magnetic Energy Storage (SMES)</p>

Back-to-back
light HVDC

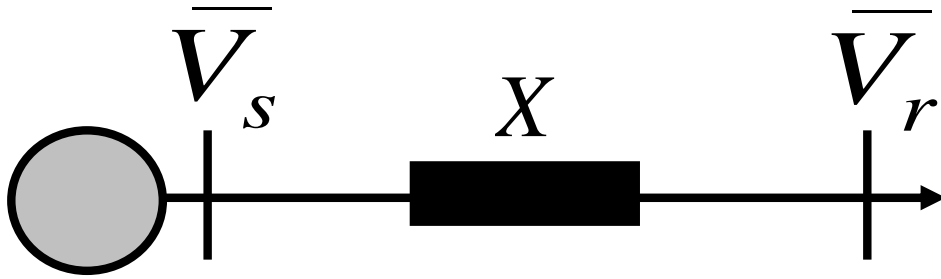
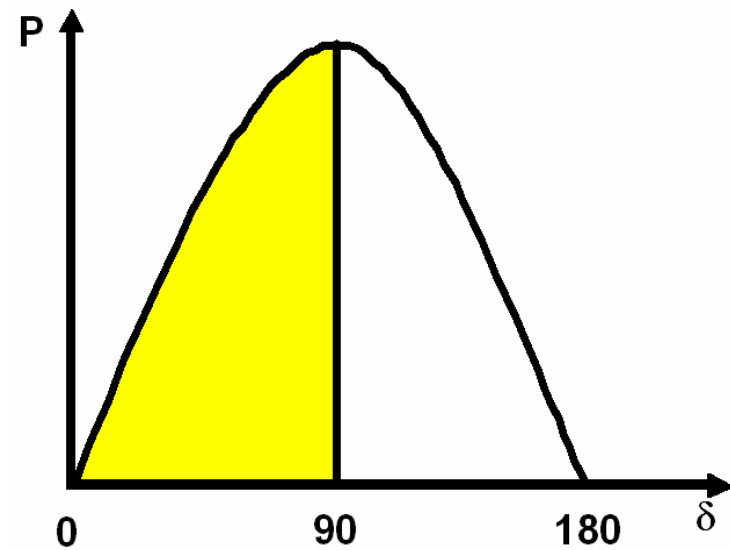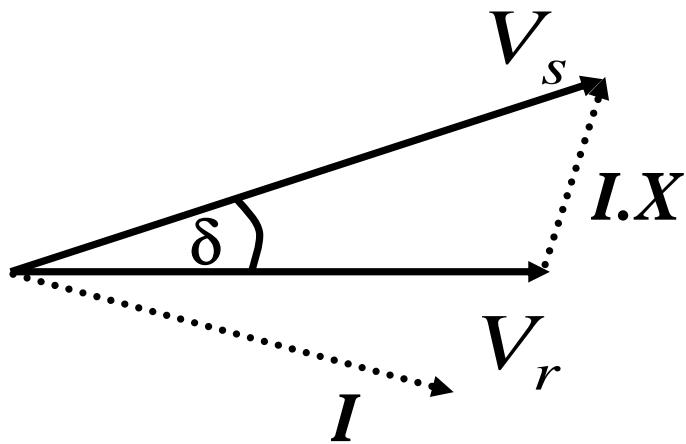
$$P = \frac{V_s \cdot V_r}{X} \sin \delta$$



Controllable parameters

Control of the line impedance

current and active power control

Control of angle

current and active power control


Series voltage injection

Current, active, and reactive power control


Parallel voltage injection

Current, active, and reactive power control


Series control

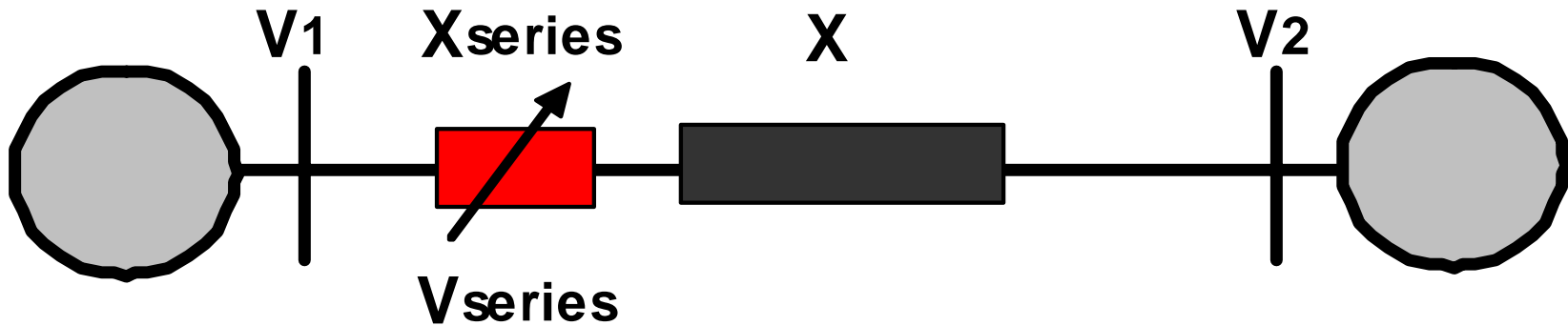

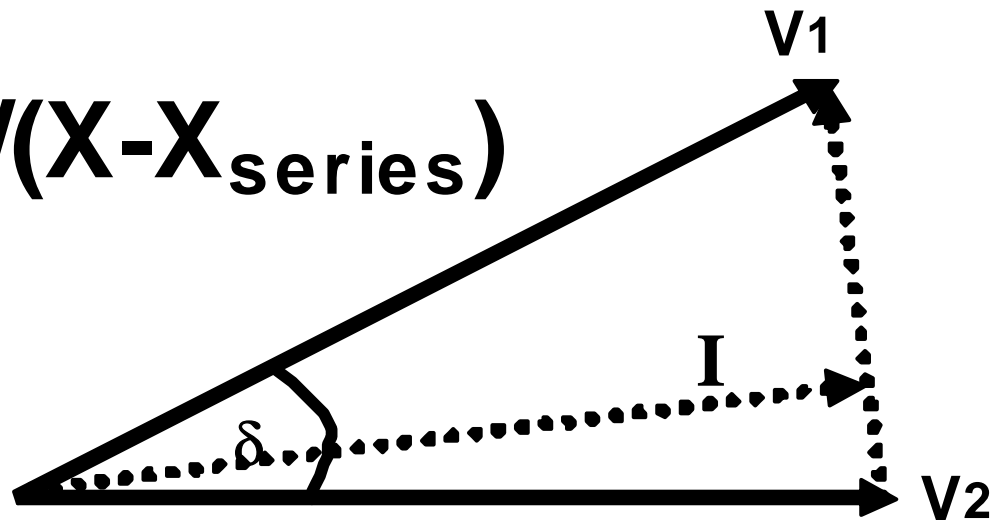
$$P = V_1 \cdot V_2 \cdot \sin(\delta) / (X - X_{series})$$




Parallel control

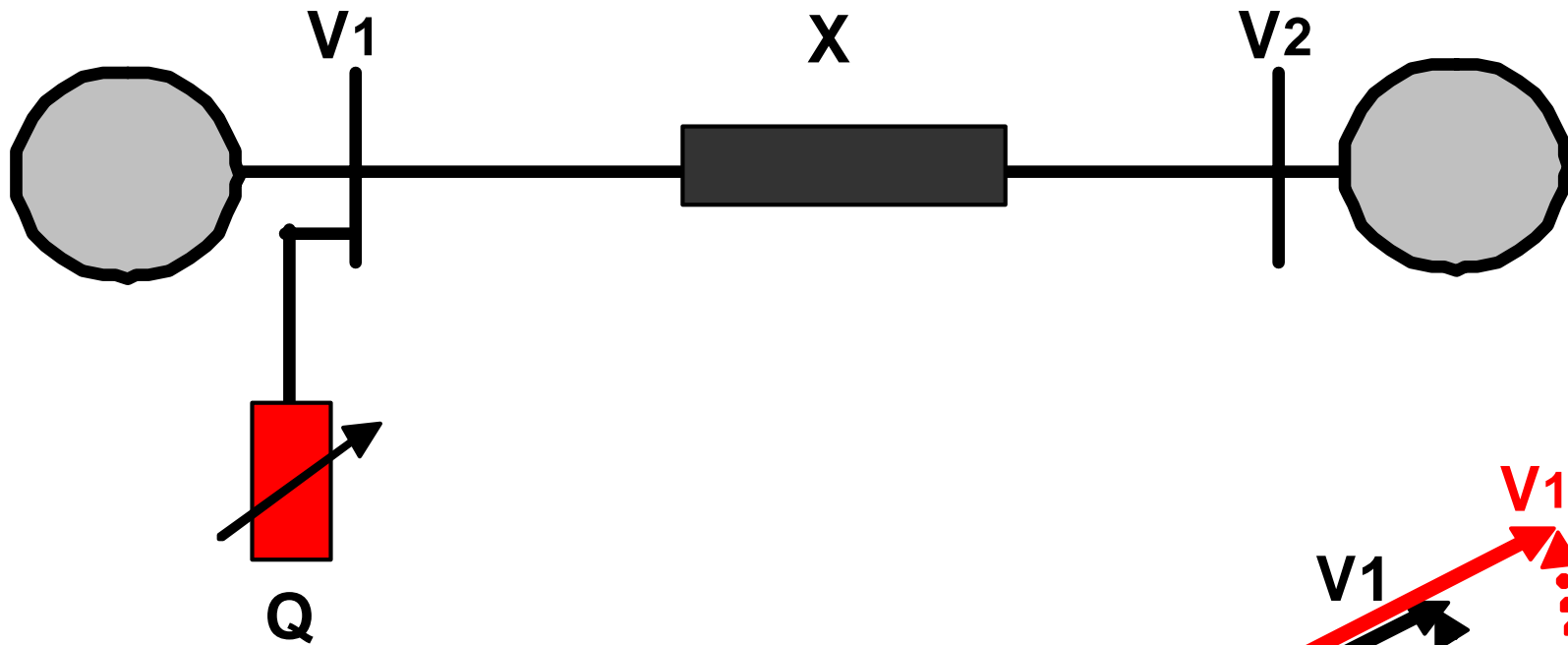
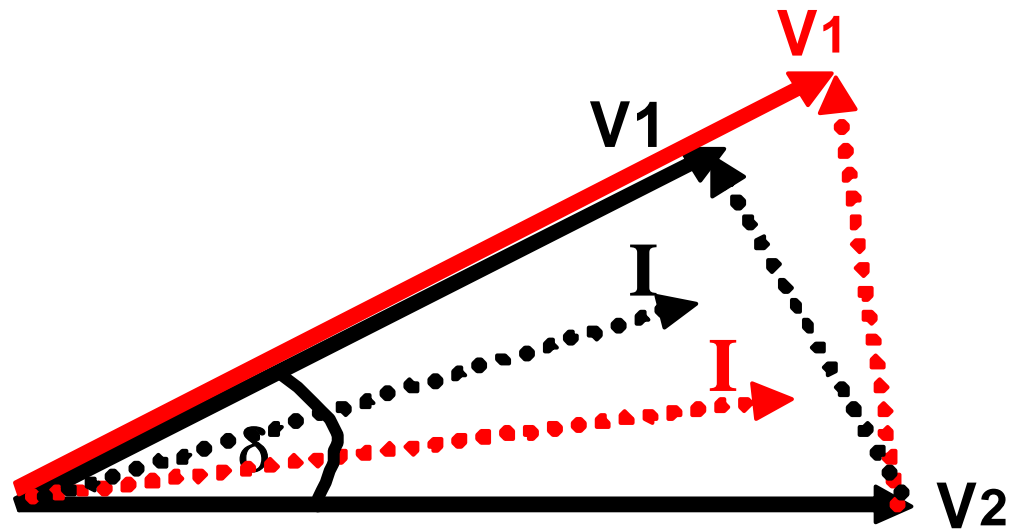
$$P = V_1 \cdot V_2 \cdot \sin(\delta) / X$$



Series and parallel control

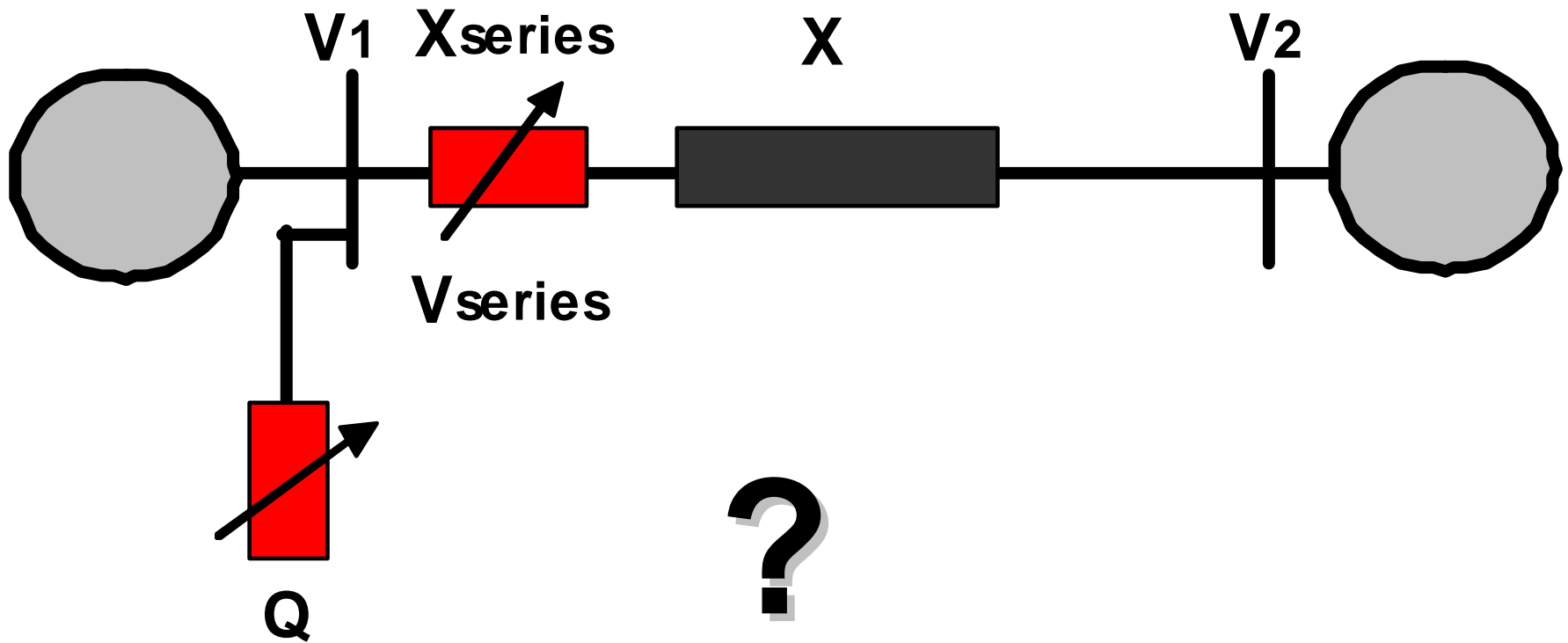

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

Static VAR compensator


- **TCR = Thyristor Controlled Reactor**
- **TSR = Thyristor Switched Reactor**
- **TSC = Thyristor Switched Capacitor**
- **MSC = Mechanically-Switched Capacitor**
- **MSR = Mechanically-Switched Reactor**
- **FC = Fixed Capacitor**
- **Harmonic Filters**

Thyristor Controlled Reactor (TCR)


Parallel-connected static var generator or absorber

- Output is adjusted to exchange capacitive or inductive current
- Maintain or control specific parameters of the electrical power system (typically bus voltage).
- Thyristor-based Controllers
- Lower cost alternative to STATCOM


Thyristor Controlled Reactor

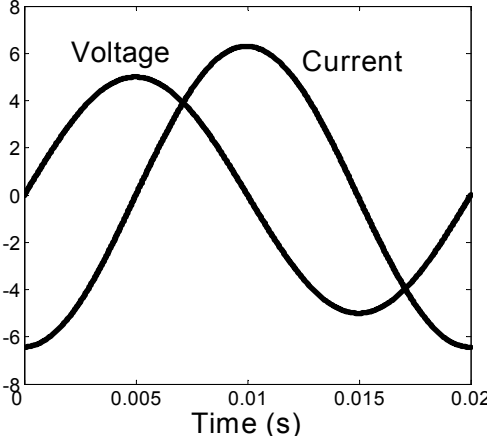


Firing angle of 90

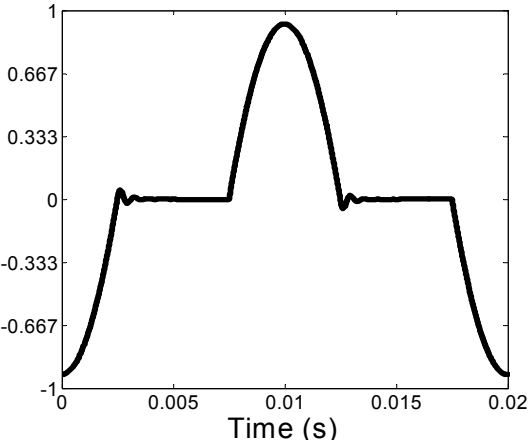

Firing angle of 135

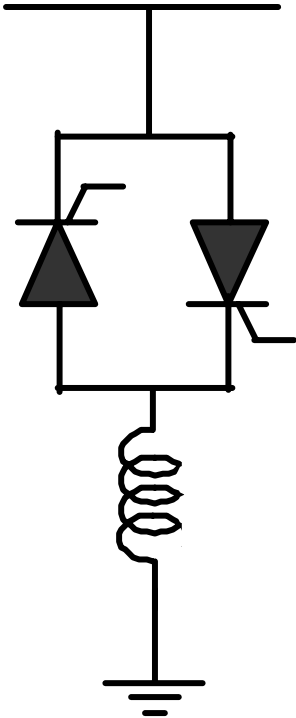


Thyristor Switched Capacitor (TSC)

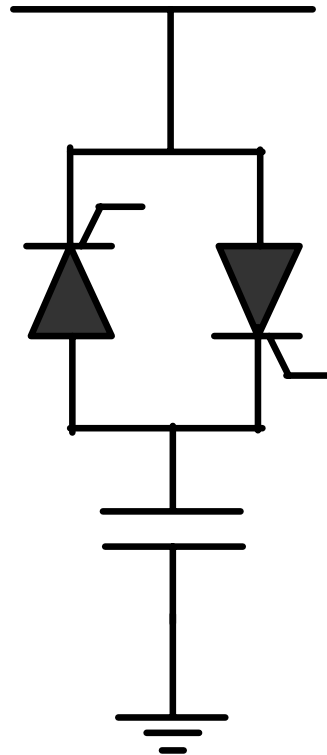


Static Synchronous Compensator (STATCOM)

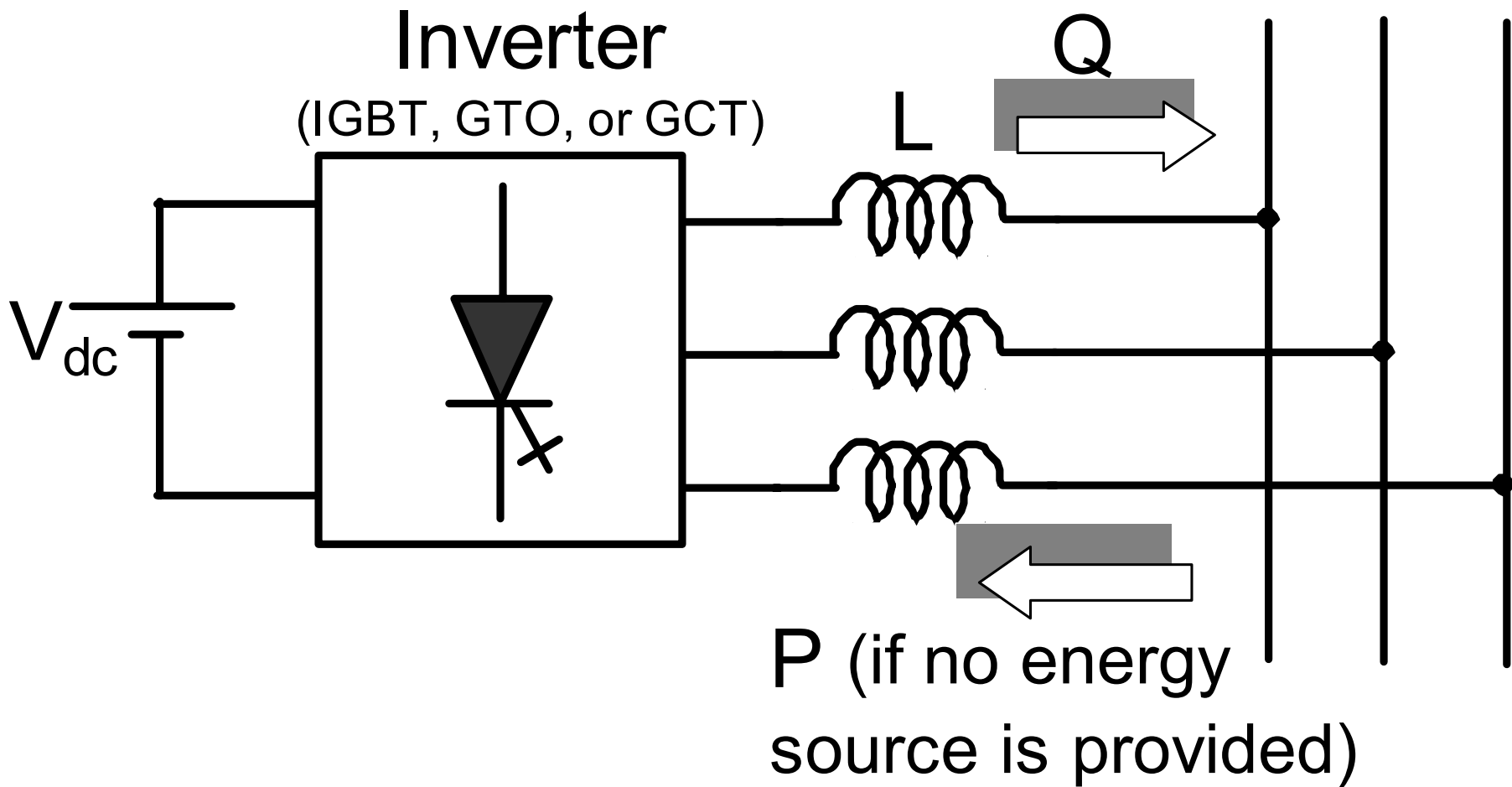- Parallel-connected static var compensator
- Capacitive or inductive output current controlled independently of the ac system voltage




Parallel Active Power Filters (Parallel APF)

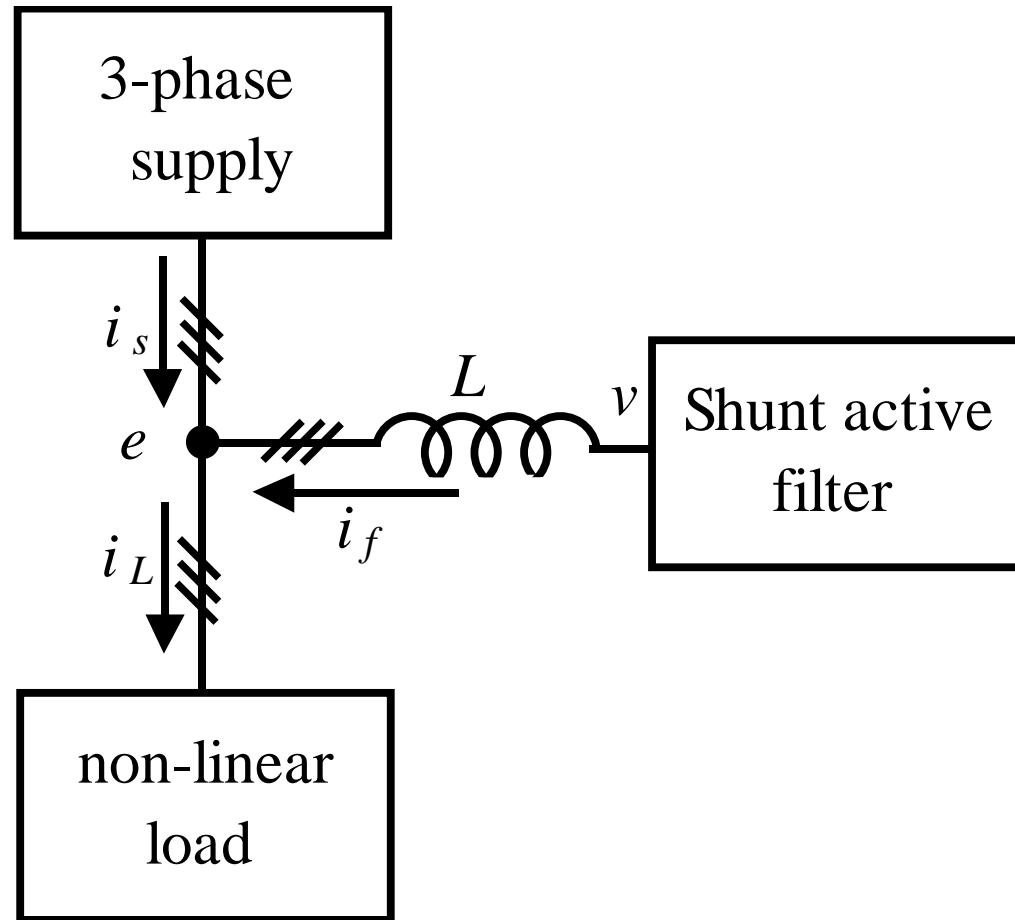
- Reactive power
- Compensation
- Source current's higher
- Harmonics compensation
- DC element voltage control



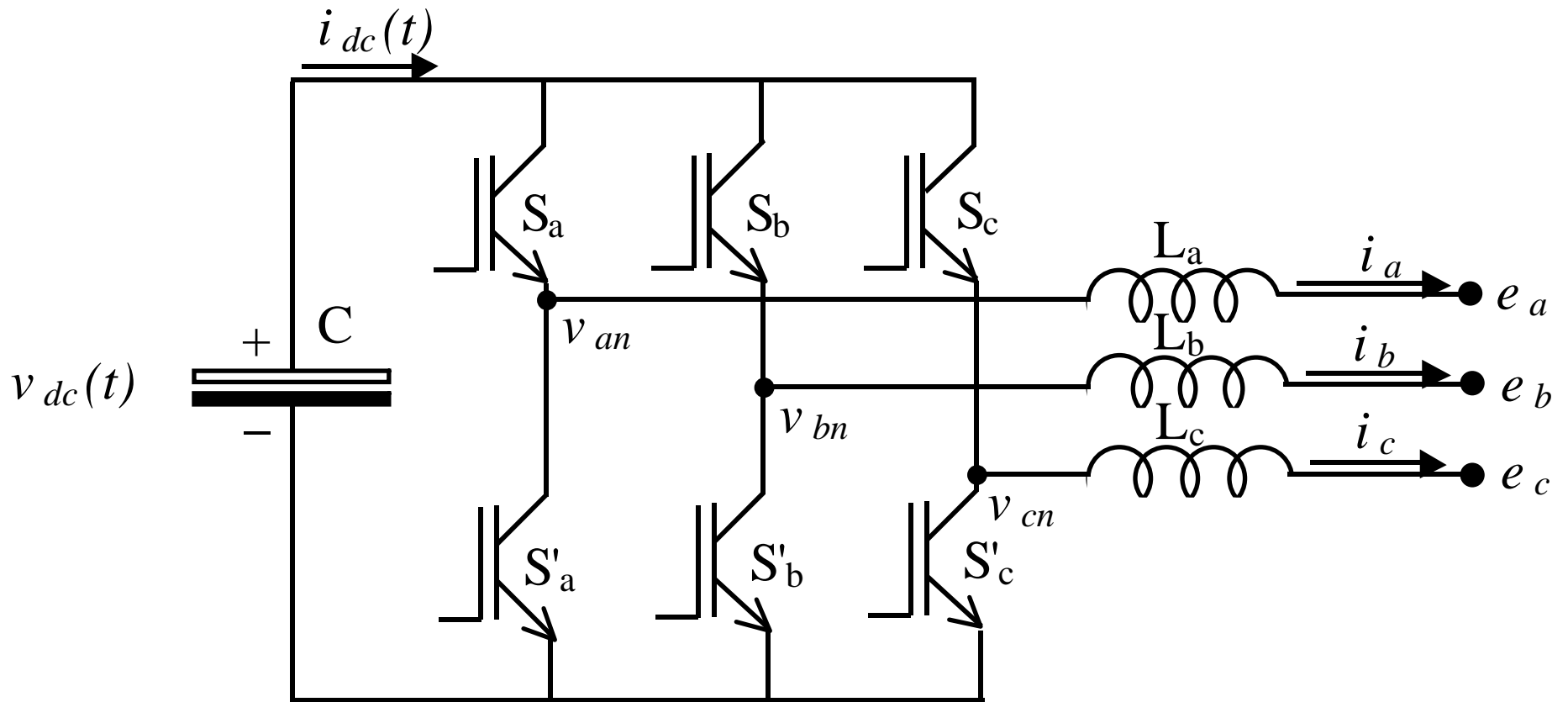Shunt active power filter single line diagram



Two level voltage source inverter

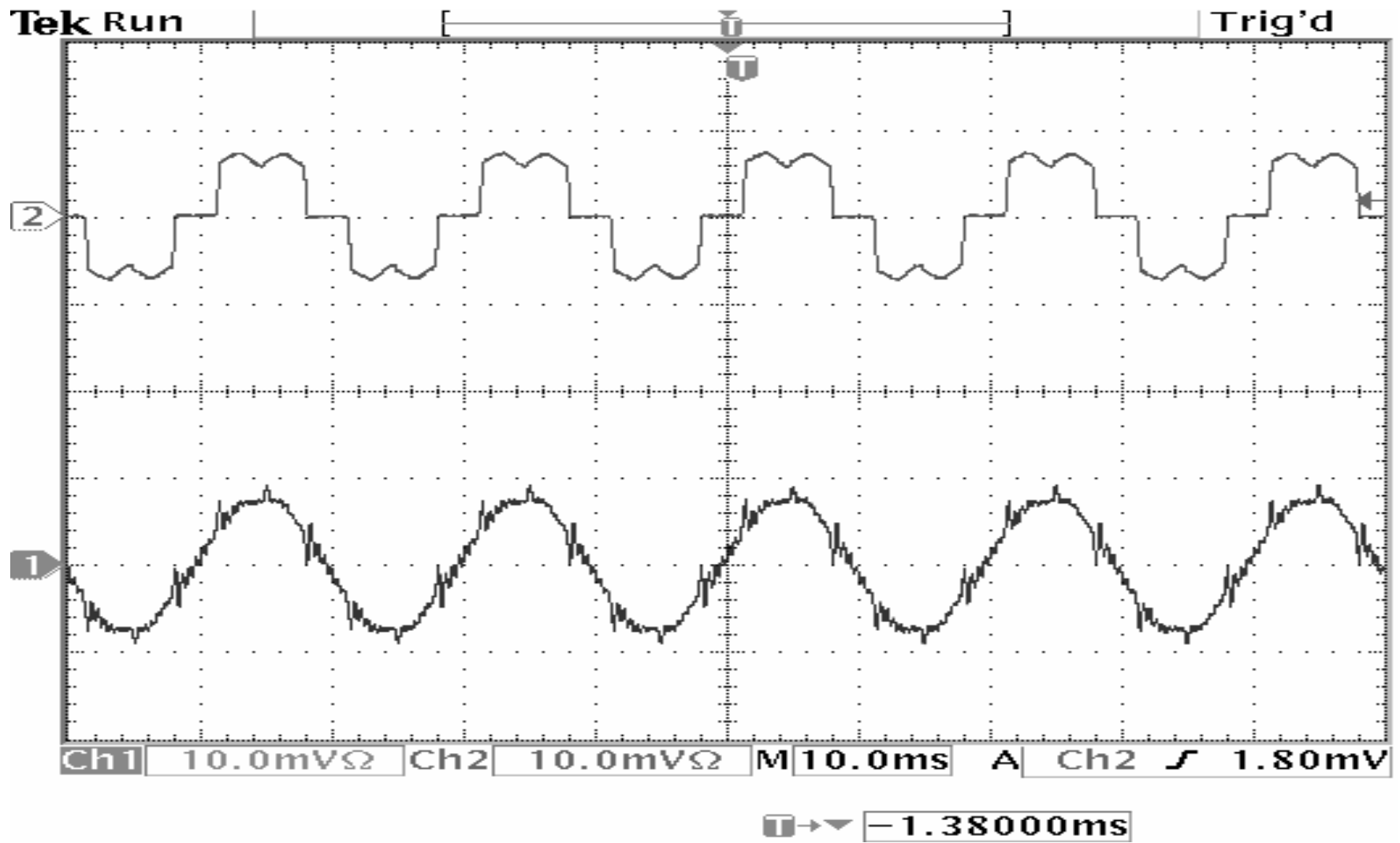

Voltage source inverters


1. Two level Voltage source inverter
2. Multilevel voltage source inverter
3. Series connection

Current source inverter ?


Multilevel inverter

1. Neutral point clamped
2. Cascaded
3. Flying capacitor


Neutral point clamped

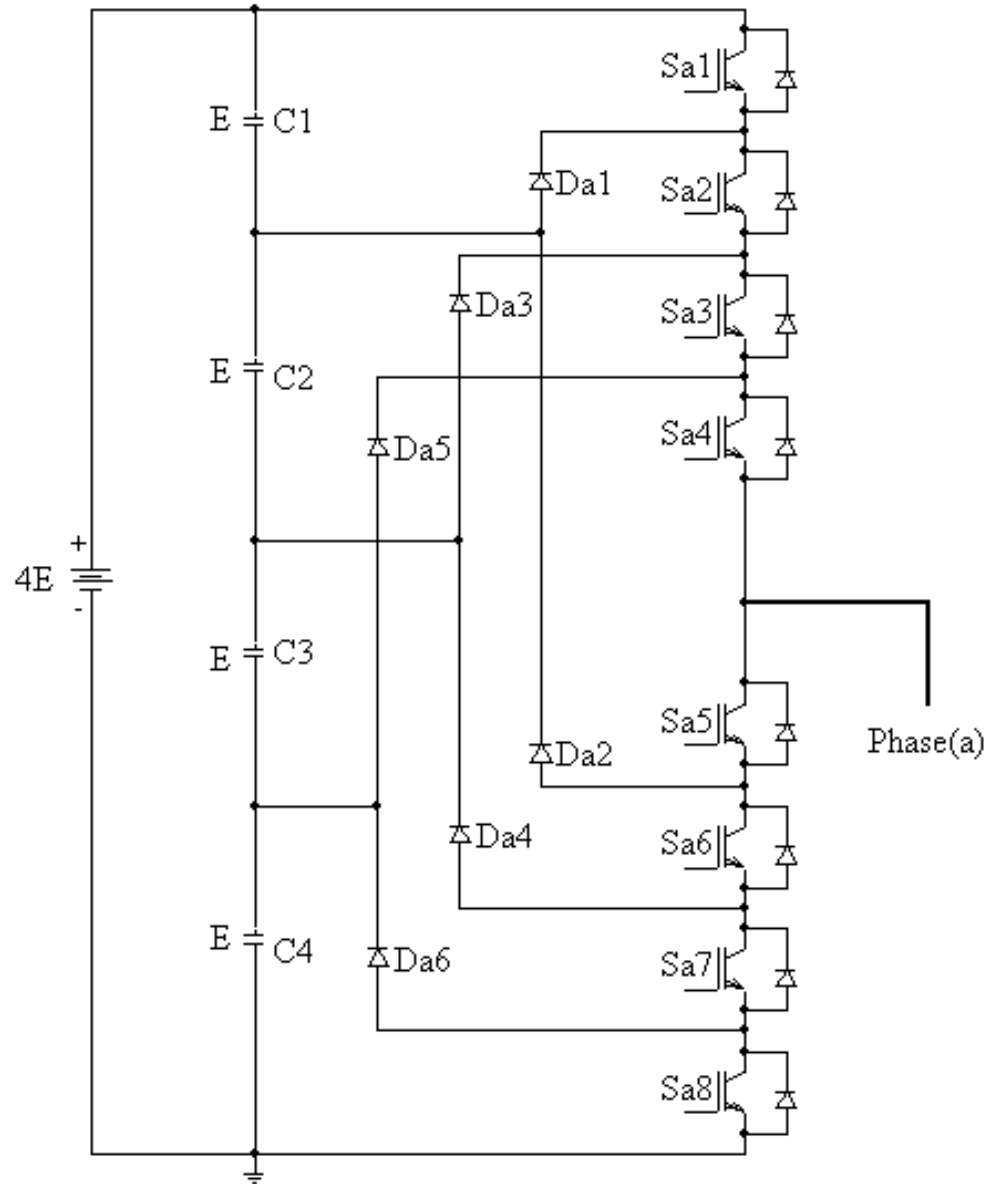





Flying capacitor

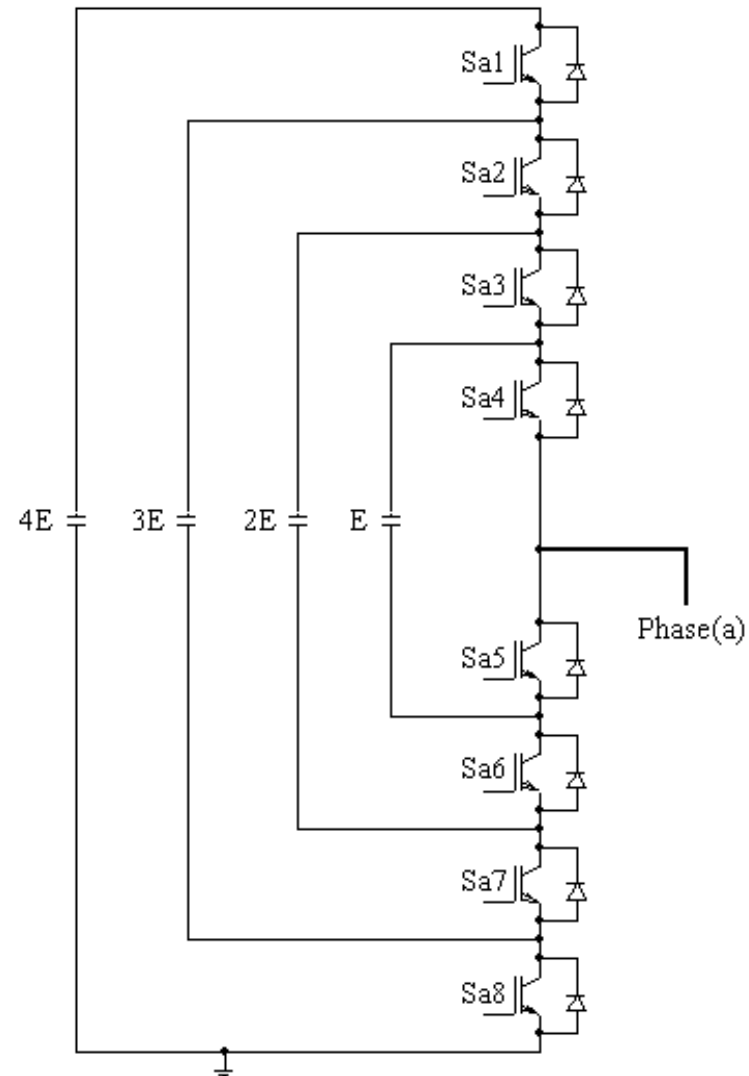

Cascaded

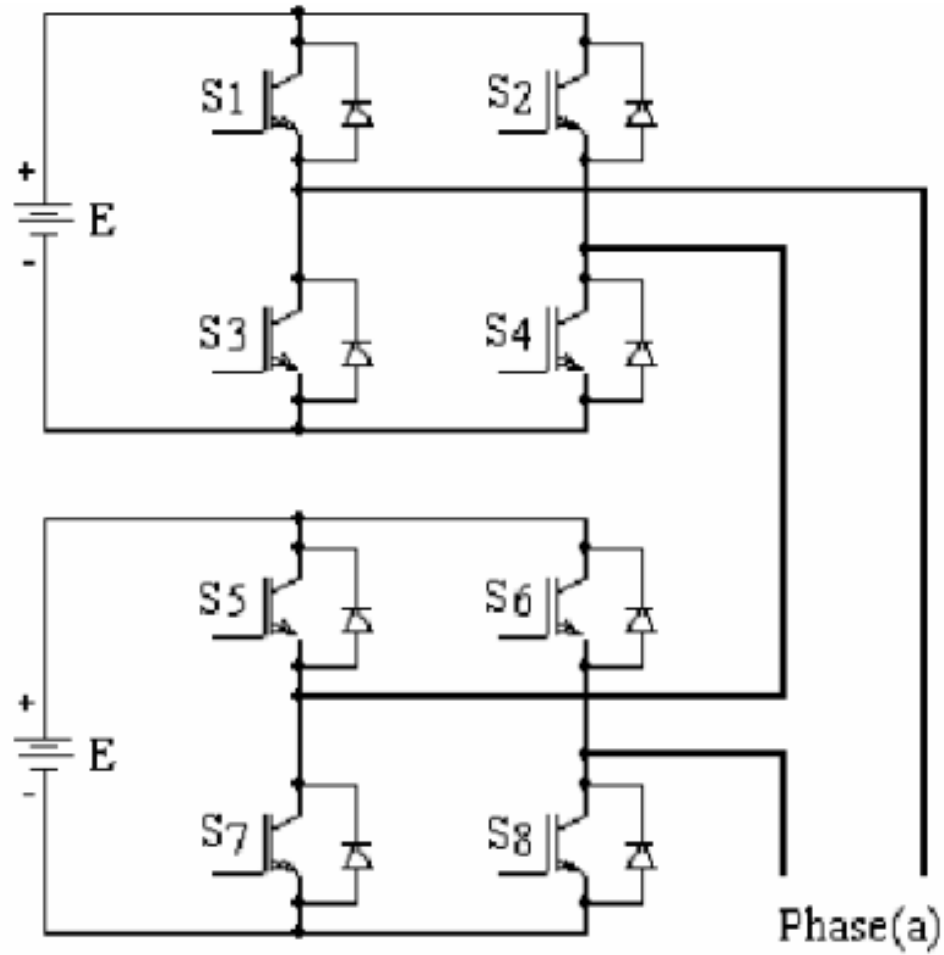


2E volt

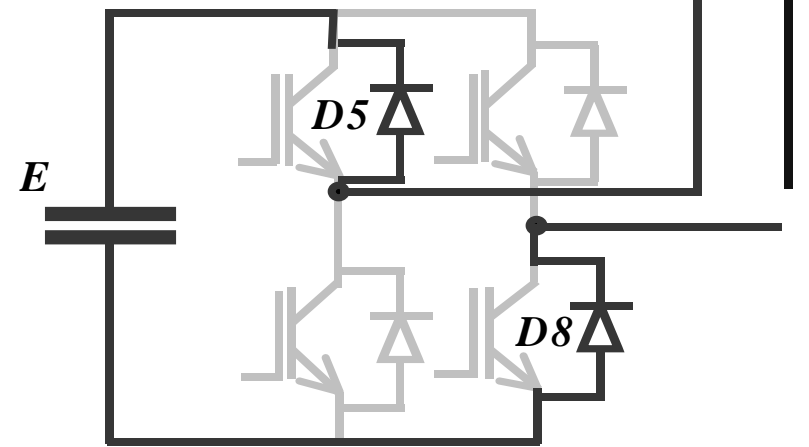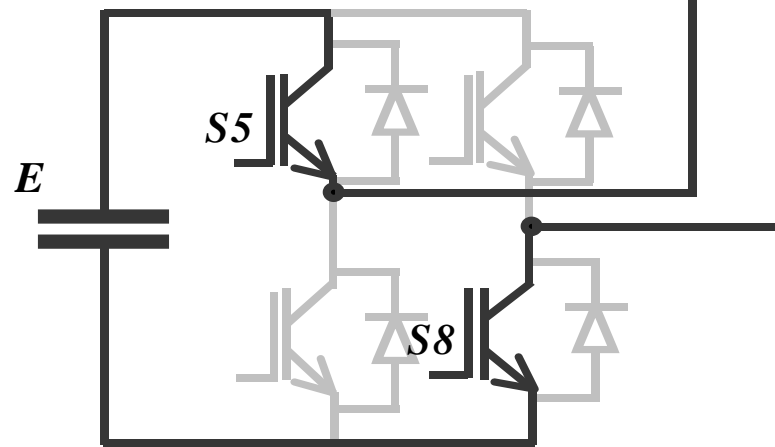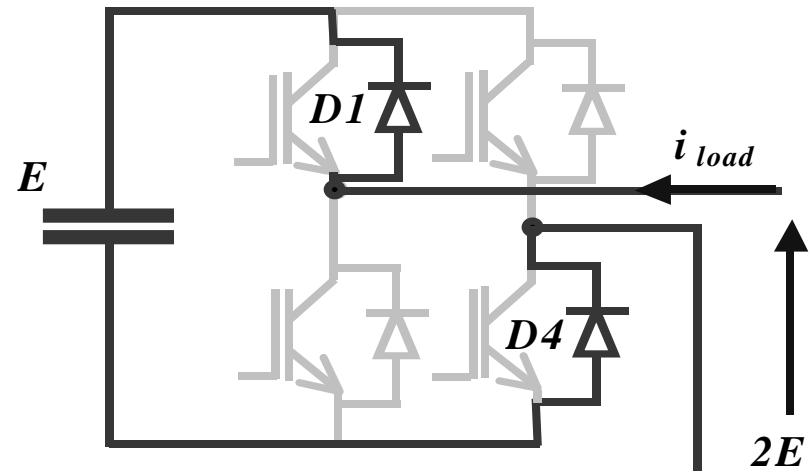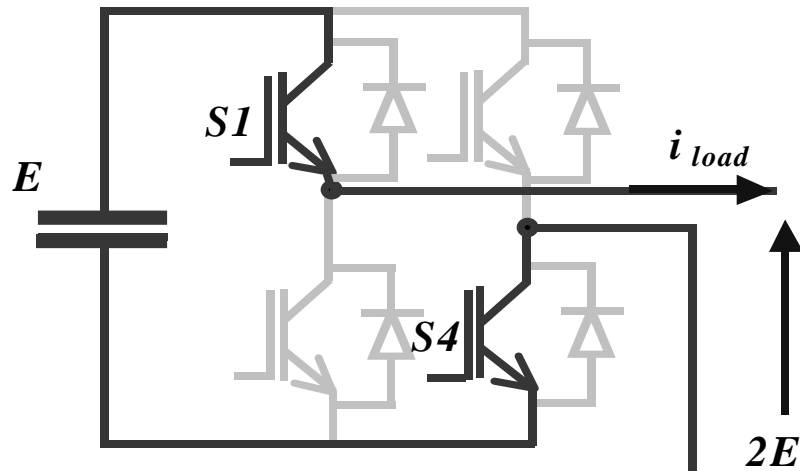


$i_{load} > 0$

$i_{load} < 0$





E volt

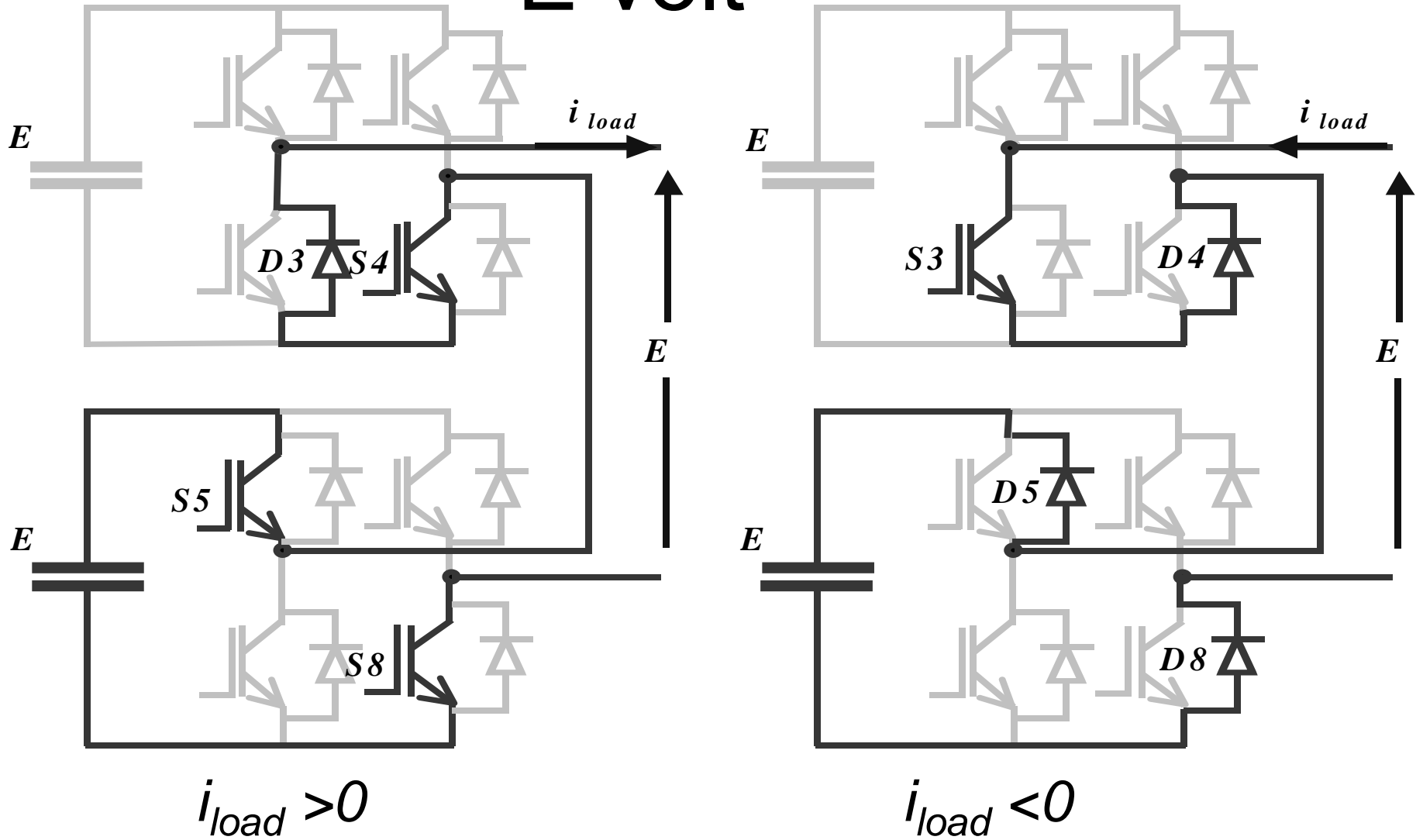

0 volt

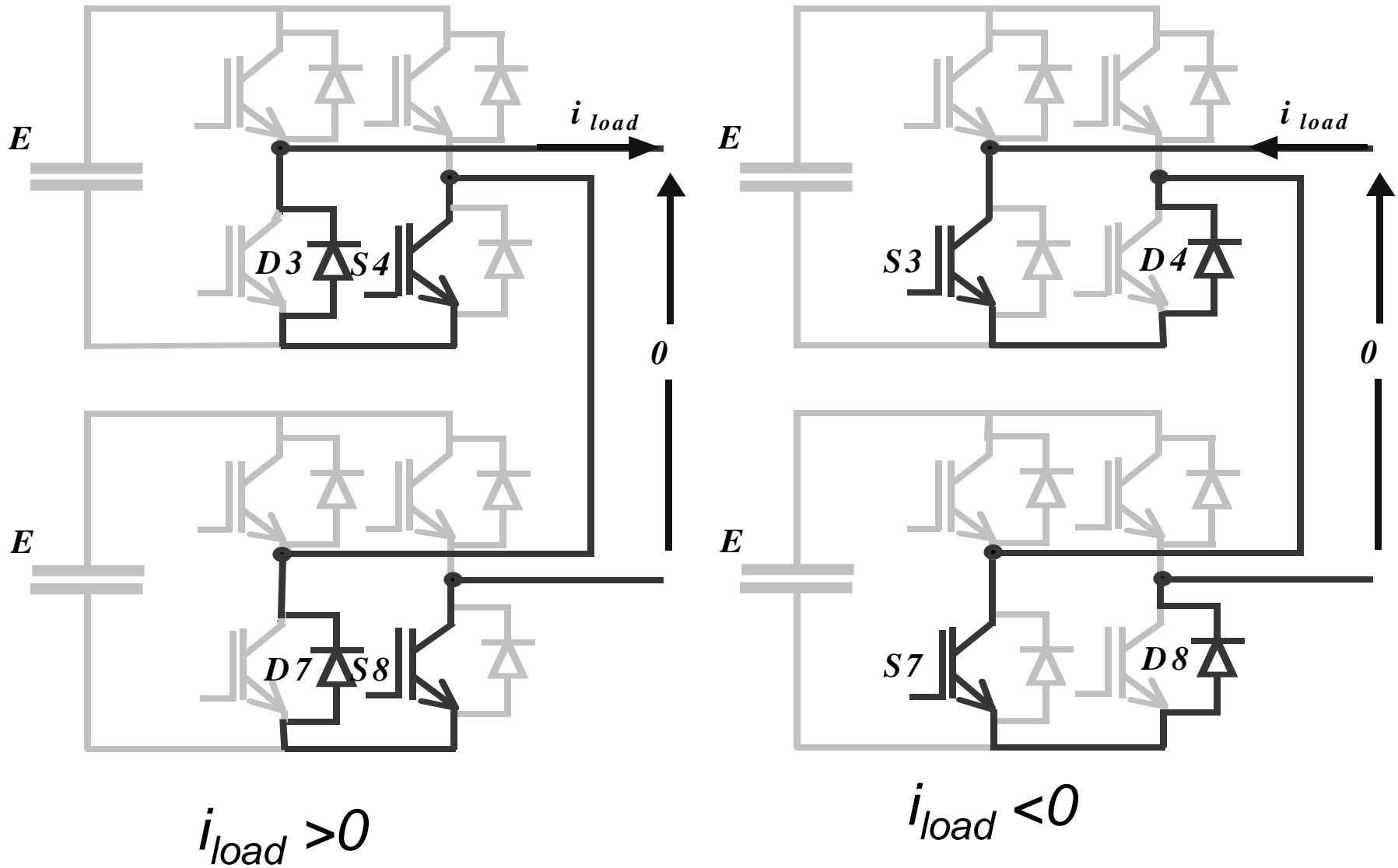


-E volt

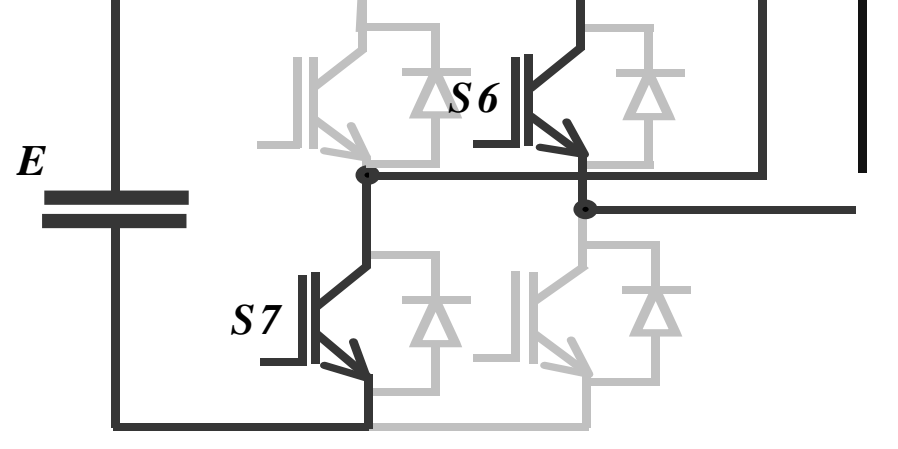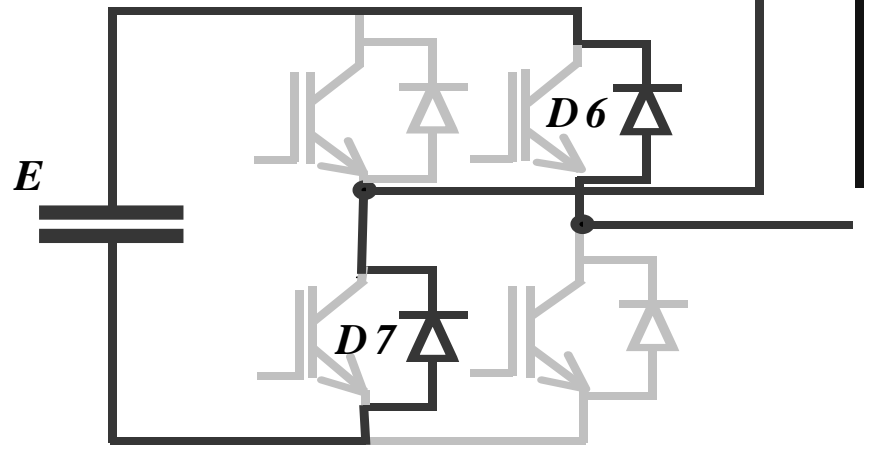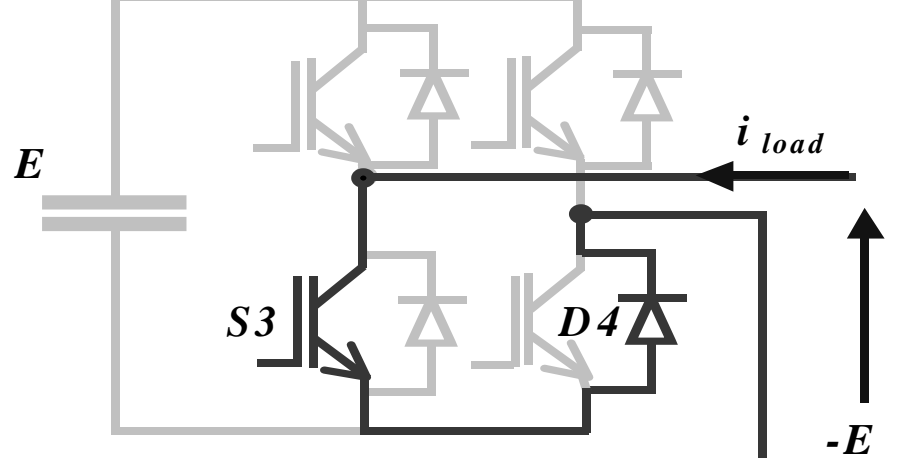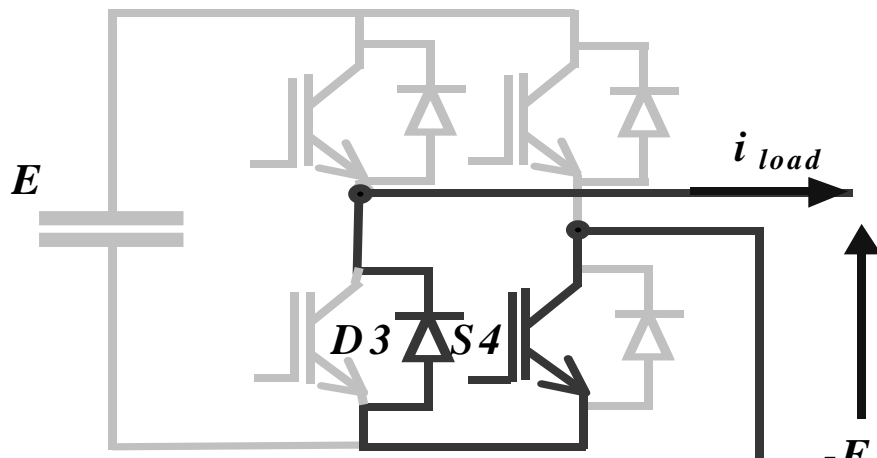


$i_{load} > 0$

$i_{load} < 0$


-2E volt

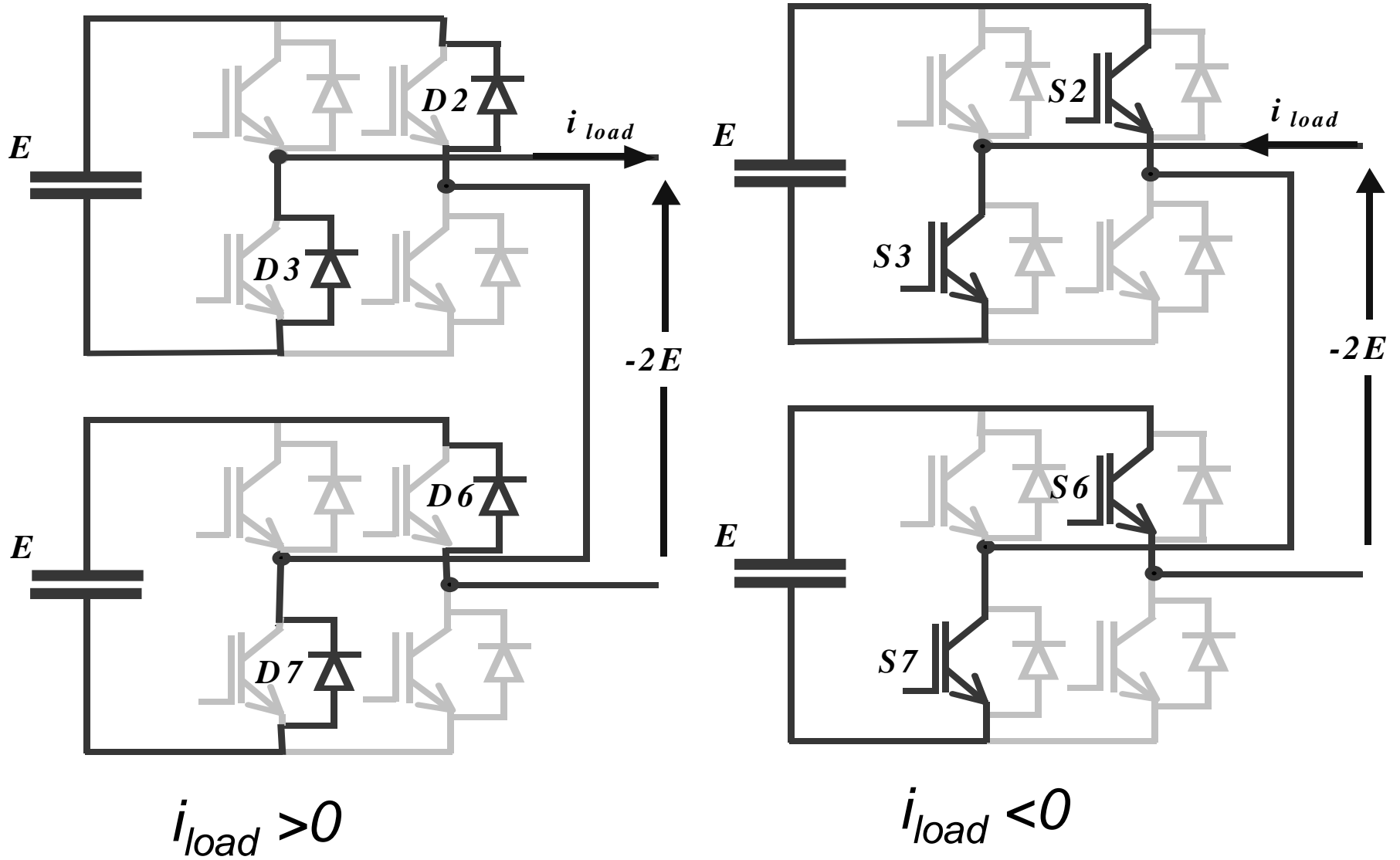


Output of 5-level inverter (PWM)

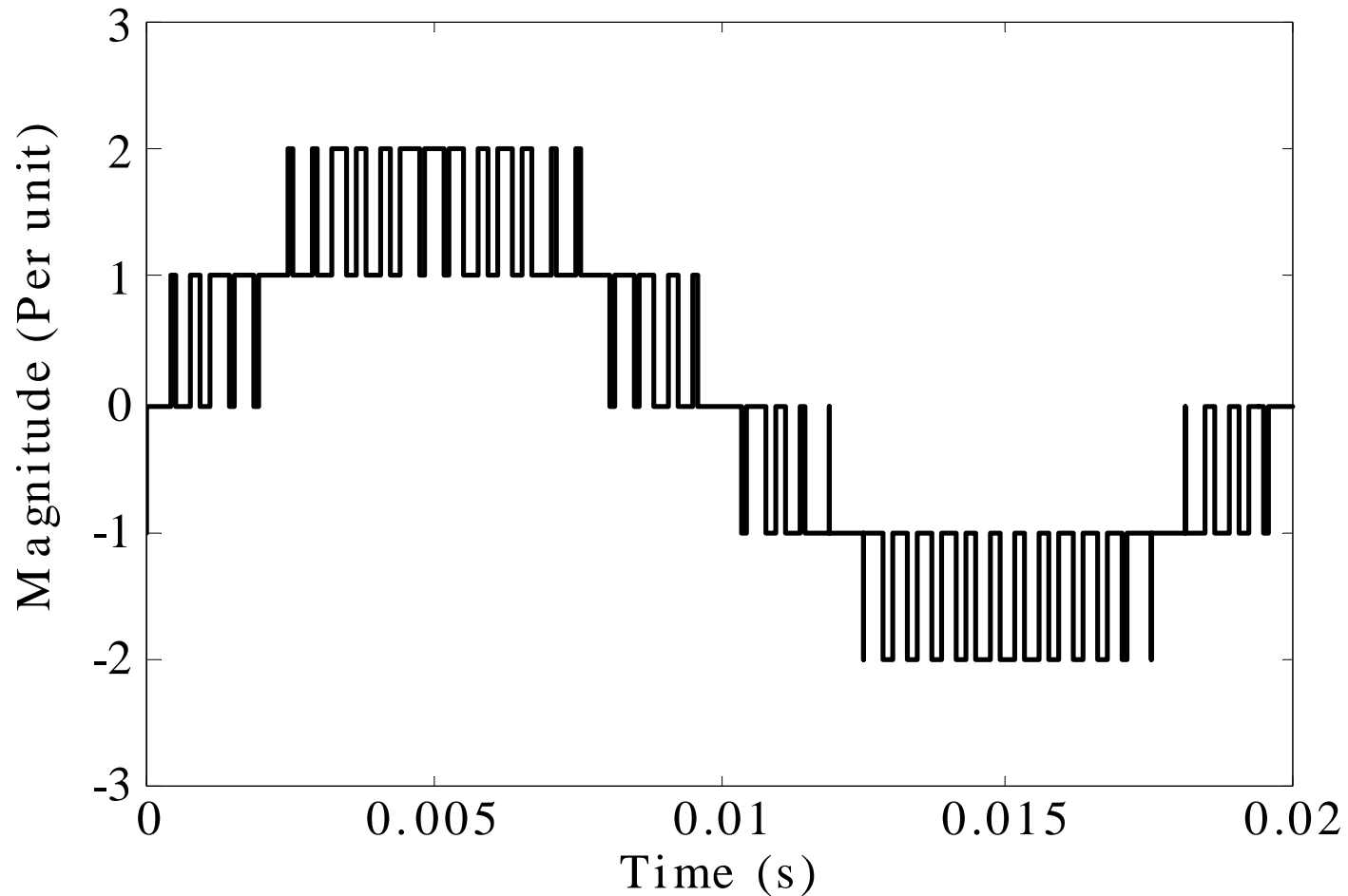

Series connection of IGBT

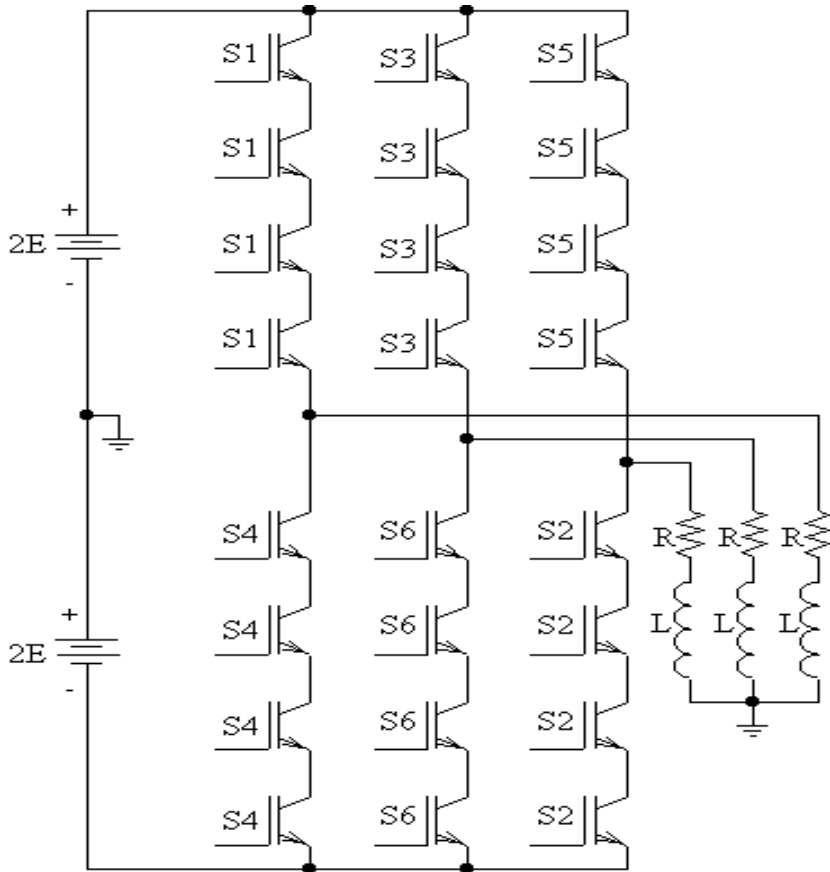

Output of two-level inverter (PWM)

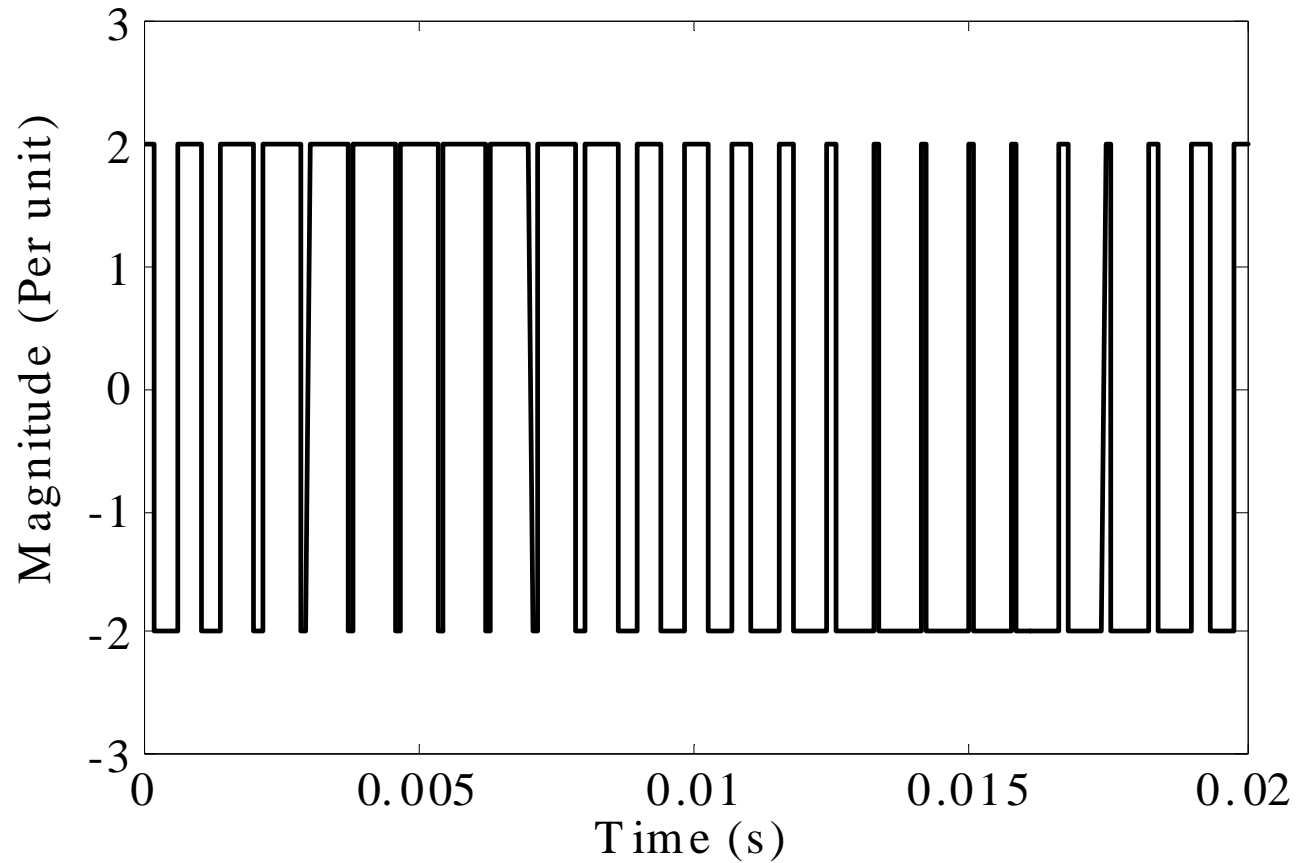

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

Series Capacitors Applied For:

Increasing Power Transfer

Increasing Stability Limits

Improving Voltage Profile

Improving Load Division

Series Active Power filter (Series APF)


- Voltage harmonics compensation
- Stability improvement
- Current harmonics blocking

Static Synchronous Series Compensator (SSSC)

- Output voltages in quadrature with, and controllable independently of, the line current
- Control the transmitted electric power.
- May include energy storage to enhance the dynamic behavior of the power system by additional temporary real power compensation, to increase or decrease momentarily, the overall real (resistive) voltage drop across the line.

Thyristor Controlled Series Capacitor (TCSC)

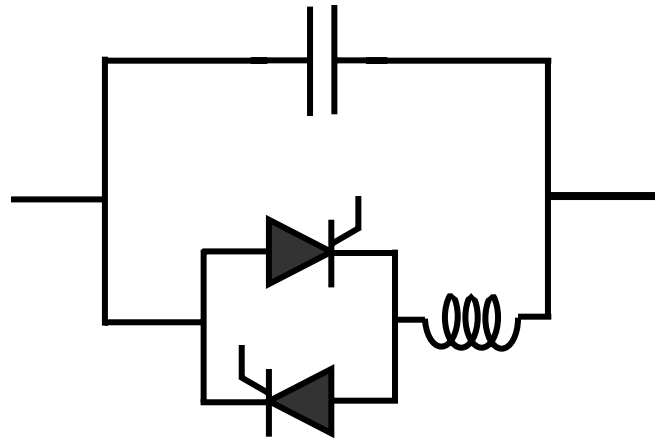- Smooth control of series capacitive reactance



FACTS


1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

Unified Power Flow Controller (UPFC)

- A combination of STATCOM and SSSC coupled via a common dc link
- Bi-directional flow of real power between the SSSC and the STATCOM

Unified Power Flow Controller = Static Synchronous Series Compensator + STATCOM


Inverter (IGBT, GTO, or GCT)

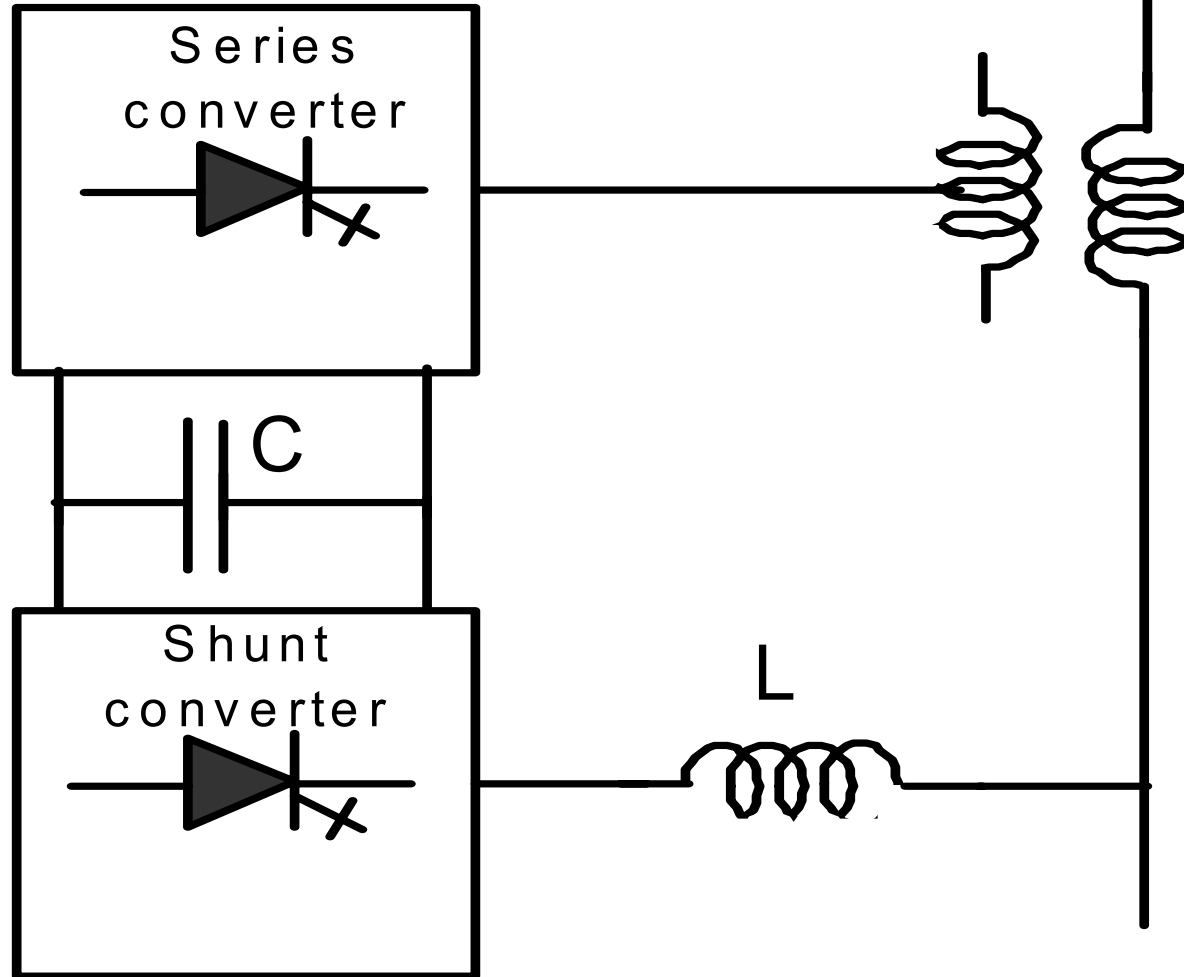


Unified Power Quality Conditioner (UPQC)

- Source current harmonics compensation
- System stability improvement
- Reactive power compensation
- DC element voltage control
- Voltage harmonics compensation

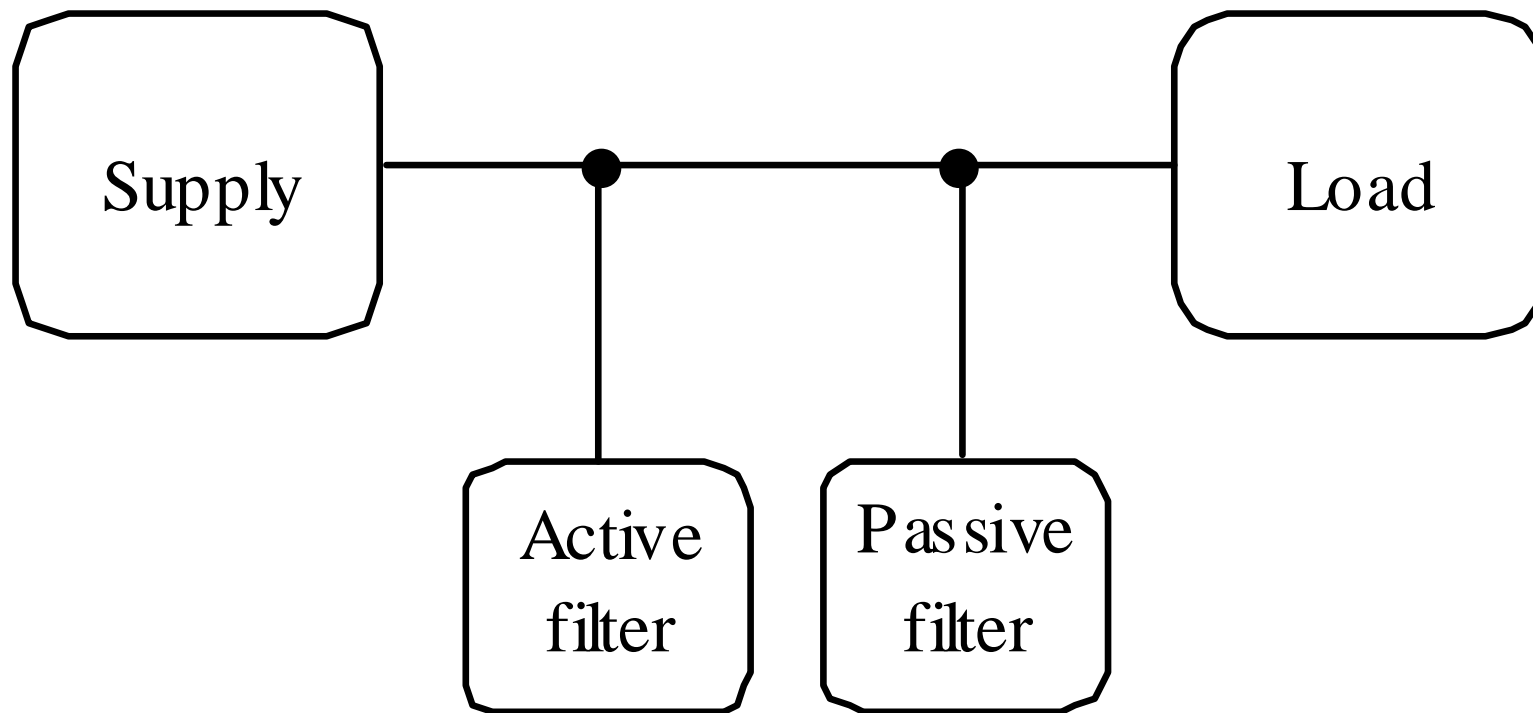
Combination of active power filter and passive filter



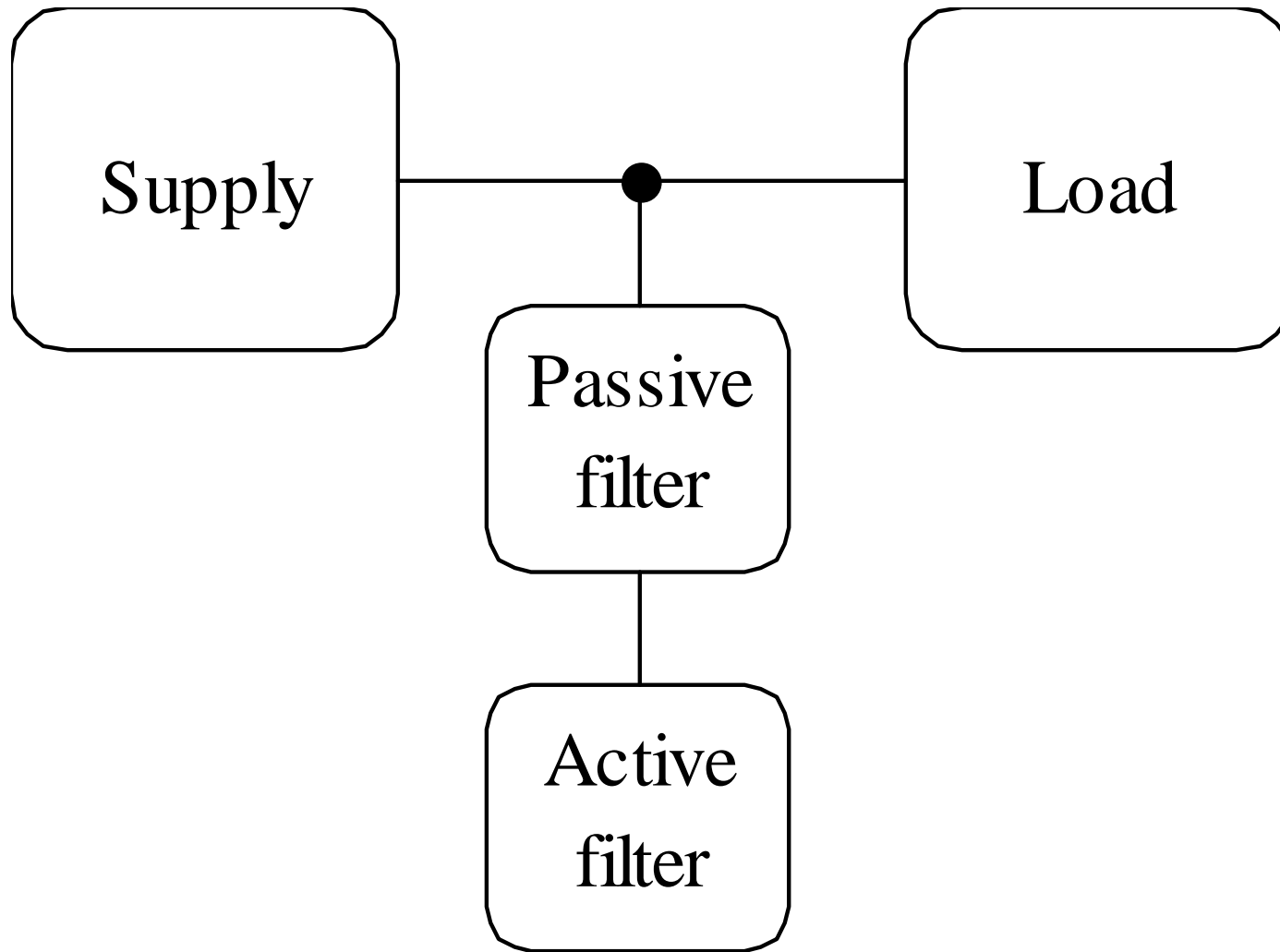
Parallel active power filter and passive filter



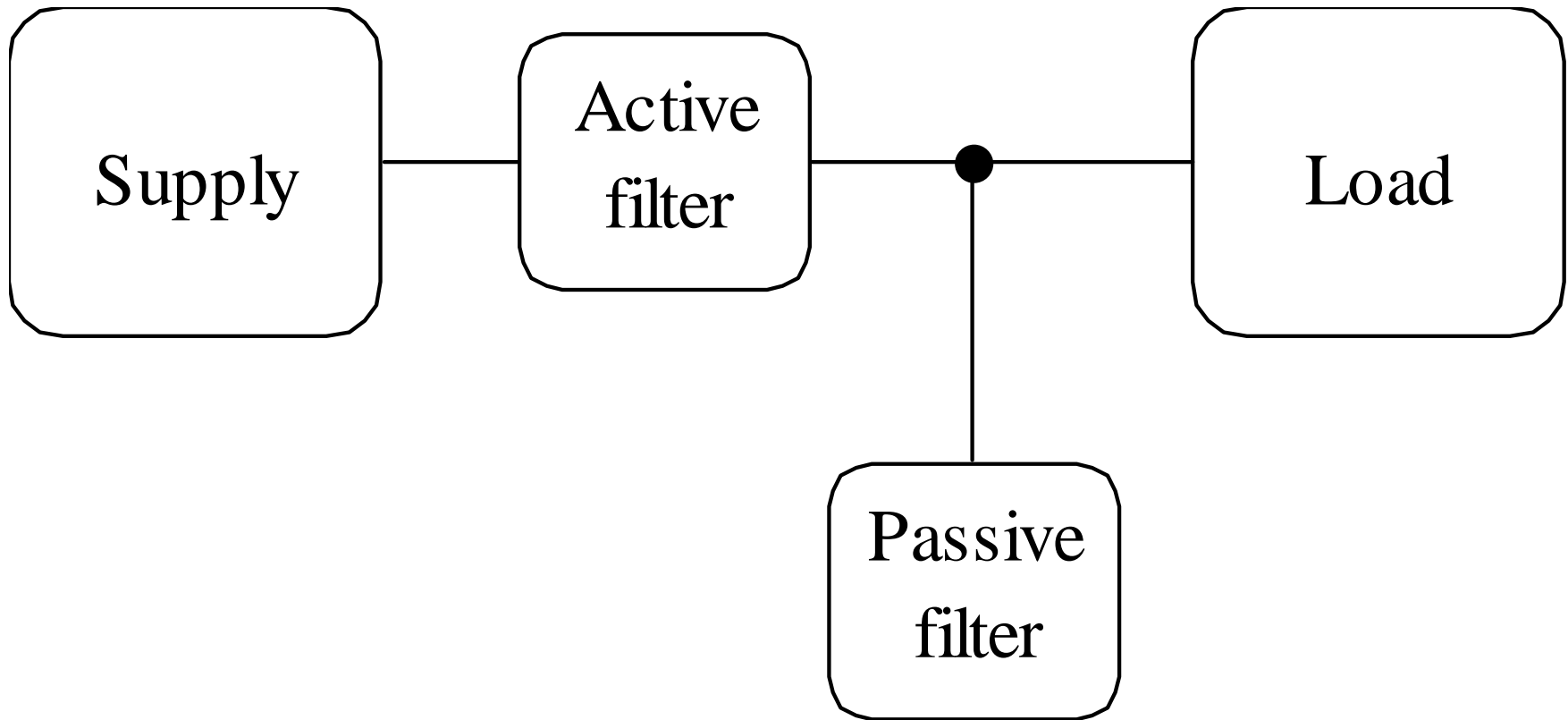Parallel active power filter in series with passive filter



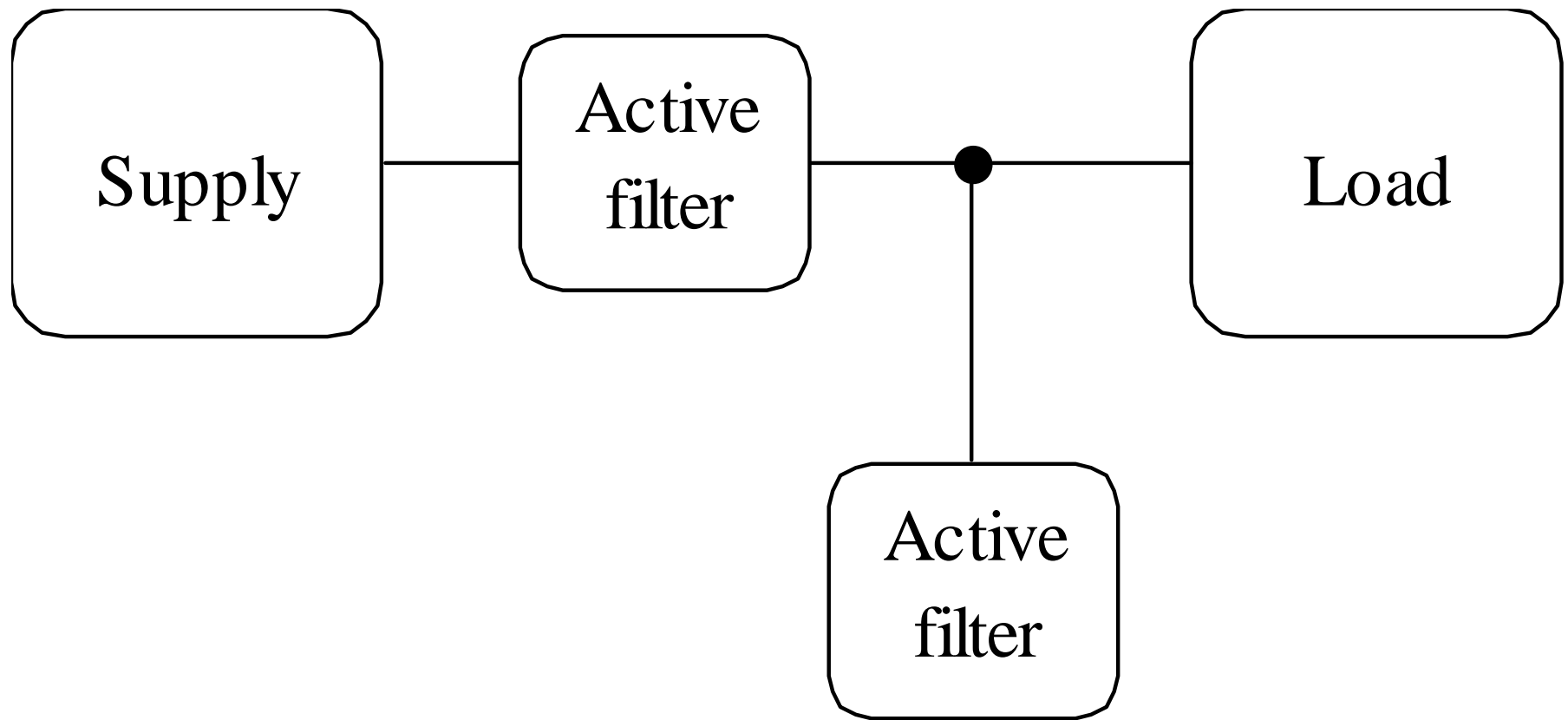Series active power filter and parallel passive filter



Series and parallel active power filter (unified power quality conditioner UPQC)


Series VS. Parallel

- Series is more powerful in controlling the current/power flow and damp oscillations
- Parallel is more effective in voltage control and damping of voltage oscillations

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

FACTS and HVDC

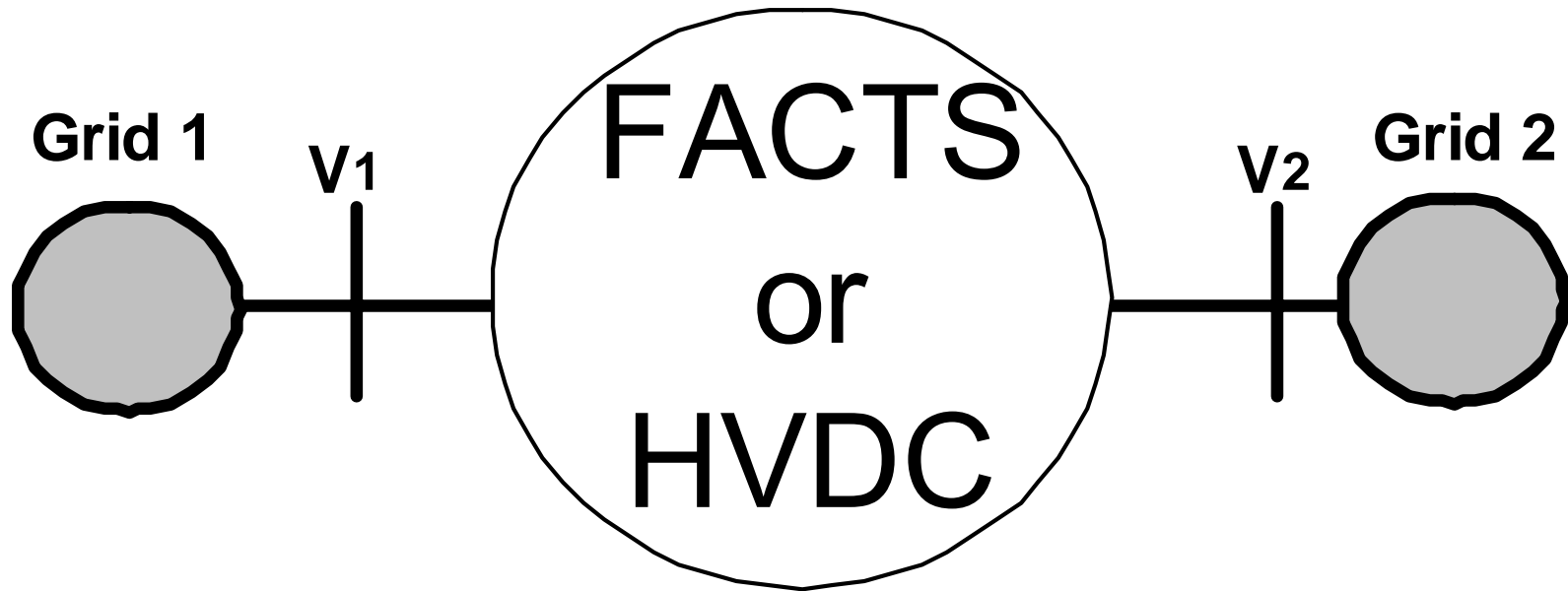


High voltage DC transmission (HVDC)

It is economically attractive:

- over a long distance from a remote generating to the load centre (>300 miles)
- underwater transmission
- when connecting two AC systems at two different frequencies

Advantages of HVDC

- No limits in transmitted distance.
- Fast control of power flow, which implies stability improvements.
- Direction of power flow can be changed very quickly.
- HVDC can carry more power for a given size of conductor
- improved transient stability
- dynamic damping of the electric system oscillations
- Require less space compared to ac for same voltage rating and size
- Ground can be used as a return conductor
- No charging current
- HVDC transmission limits short circuit currents

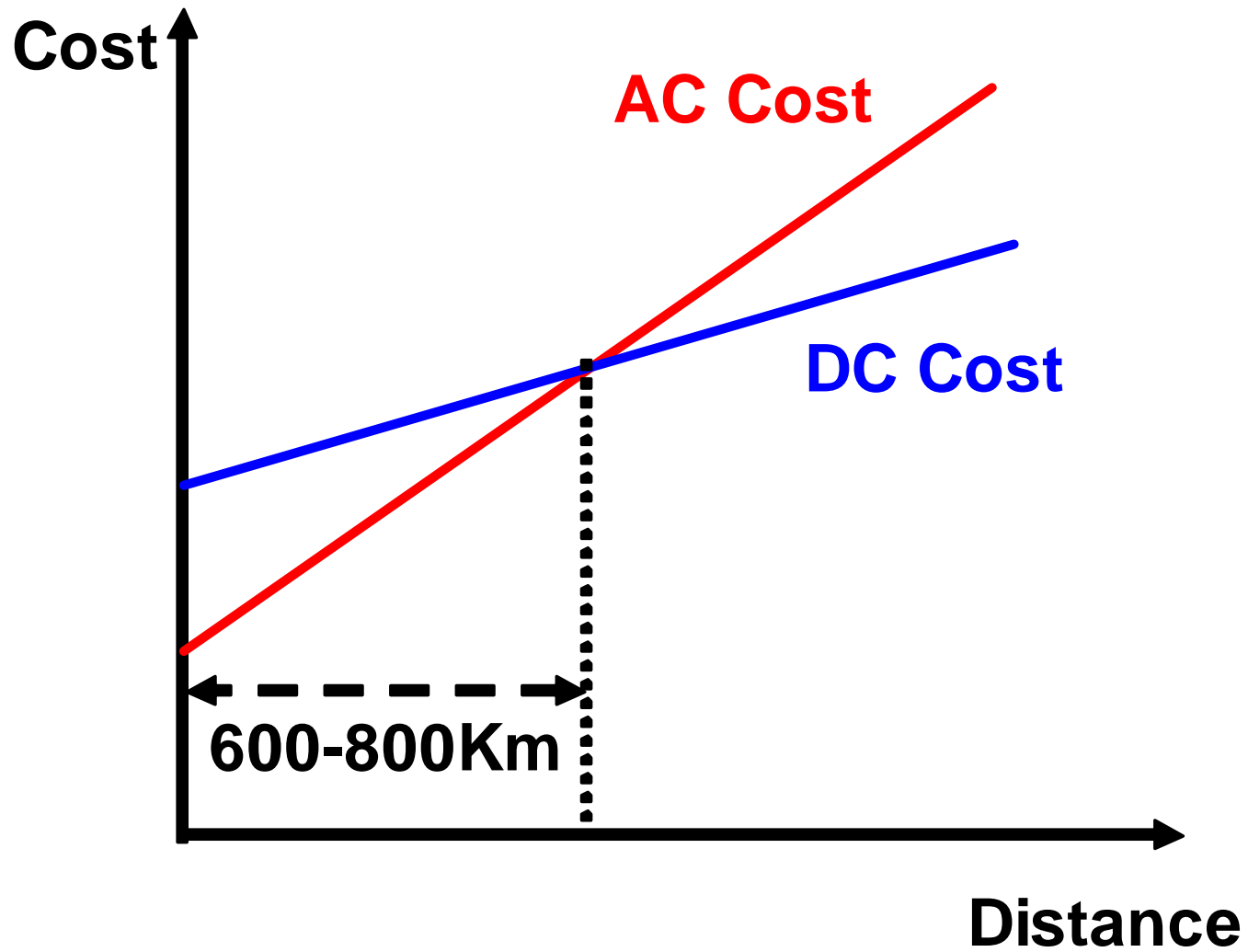


The HVDC technology

The fundamental process that occurs in an HVDC system is the conversion of electrical current from AC to DC (rectifier) at the transmitting end, and from DC to AC (inverter) at the receiving end.

1. Natural Commutated Converters. The component that enables this conversion process is the thyristor (high power and low switching frequency).
2. Forced Commutated Converters. It uses GTO or IGBT. They are known as VSC (Voltage Source Converters).

HVDC transmission system

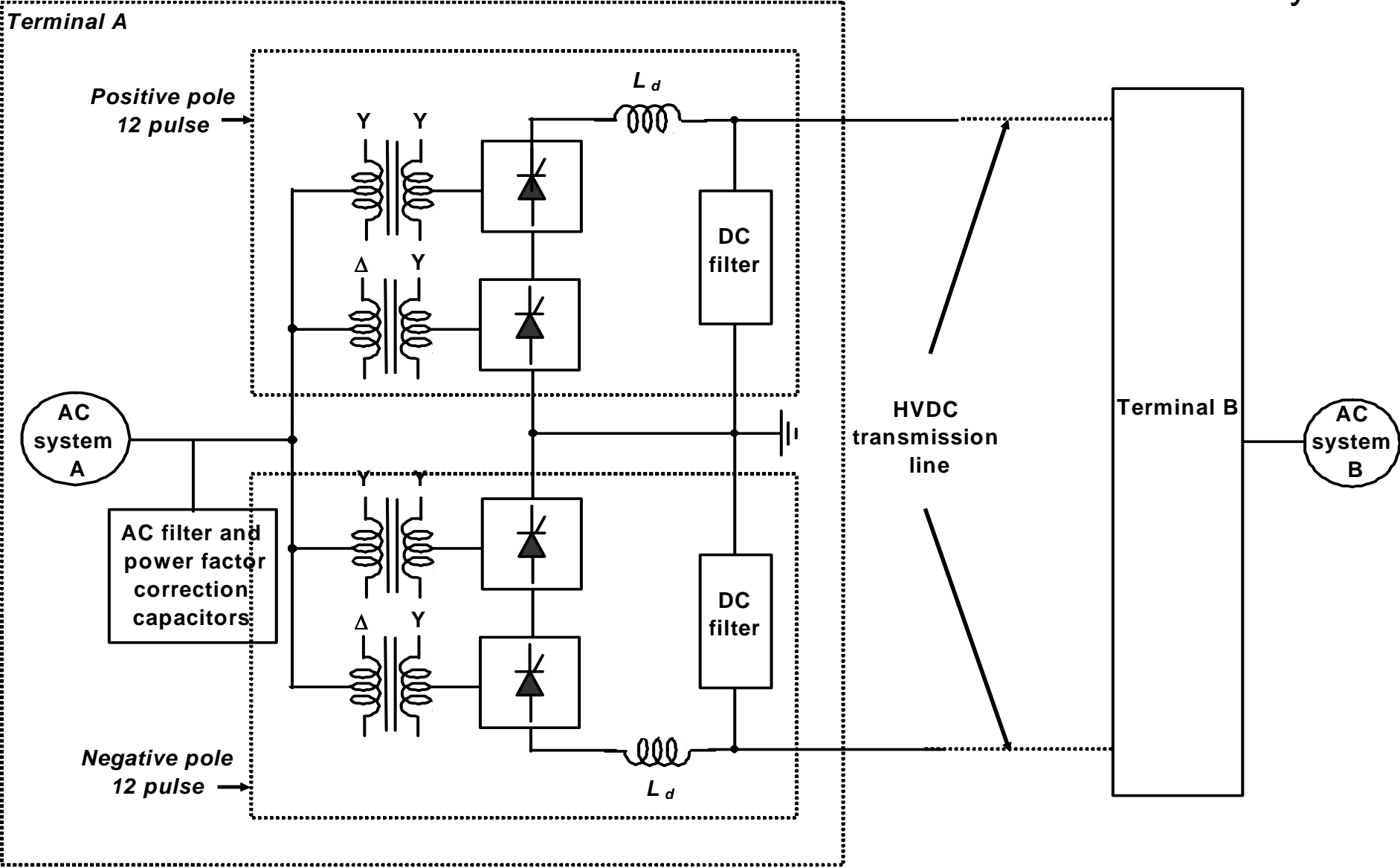

Components of HVDC

1. Converter: at one side rectifier and the other inverter each converter consists of a positive pole and a negative pole each pole consists of 6 pulse converters connected through star-delta and star-star transformer to yield 12 pulse converter
2. On the AC side:
 - * AC filters to reduce the current harmonics generated from the converters
 - * Power factor correction capacitors to supply the lagging reactive power
3. On the DC side: smoothing reactor and DC filters to filter the ripple in the DC currents


12 pulse line frequency converter

Objectives:

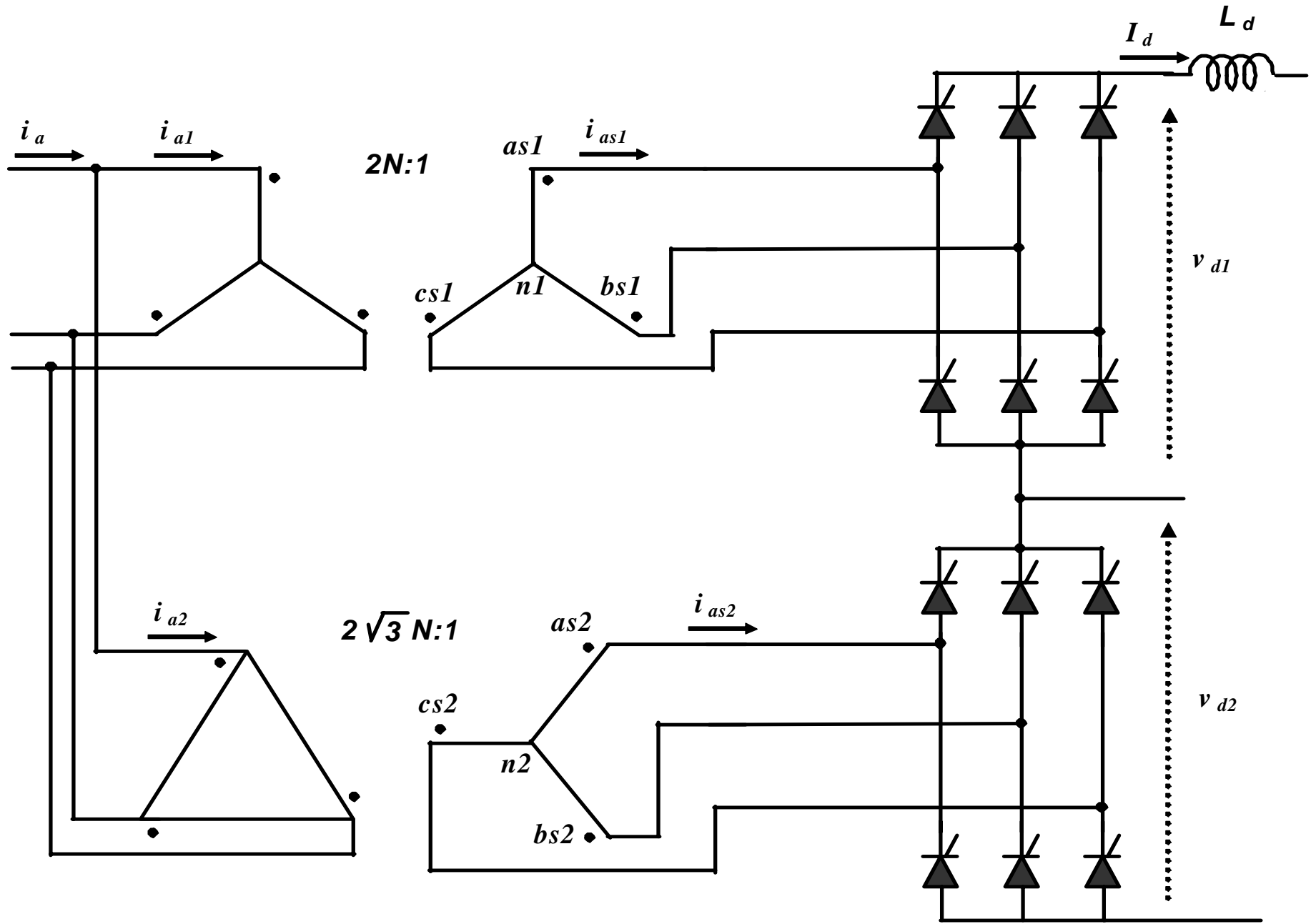1. Reduce current harmonics on AC side
2. Reduce voltage ripple on DC side
3. High power


12 pulse converter consists of two six-pulse converters connected through star-star and delta-star transformer

The 2 converters are connected in series from the DC side and parallel from the AC side




Types of HVDC links

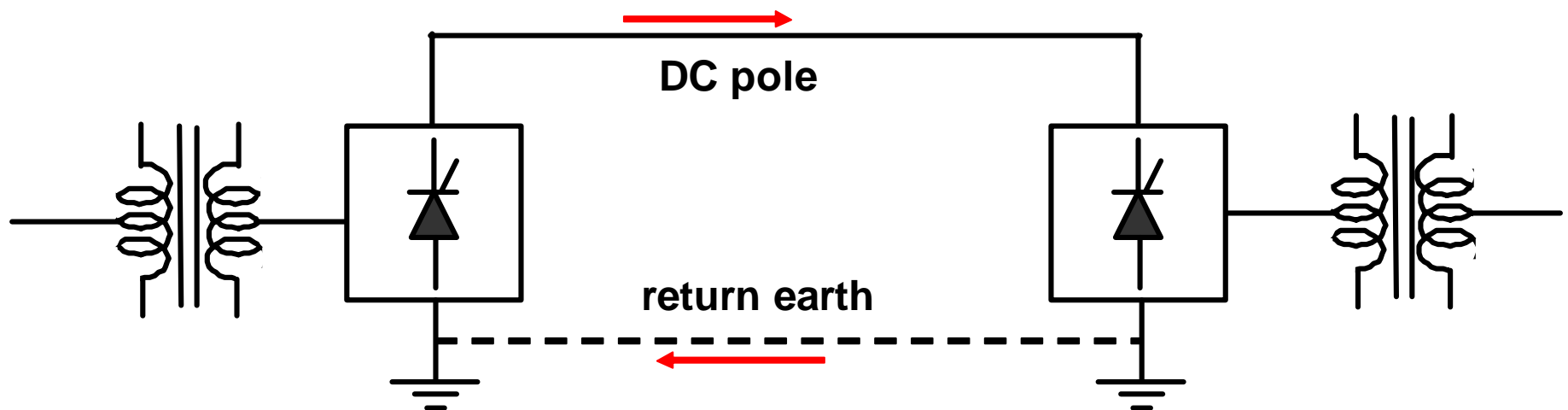1. Monopolar: Having one conductor and the ground is the return path



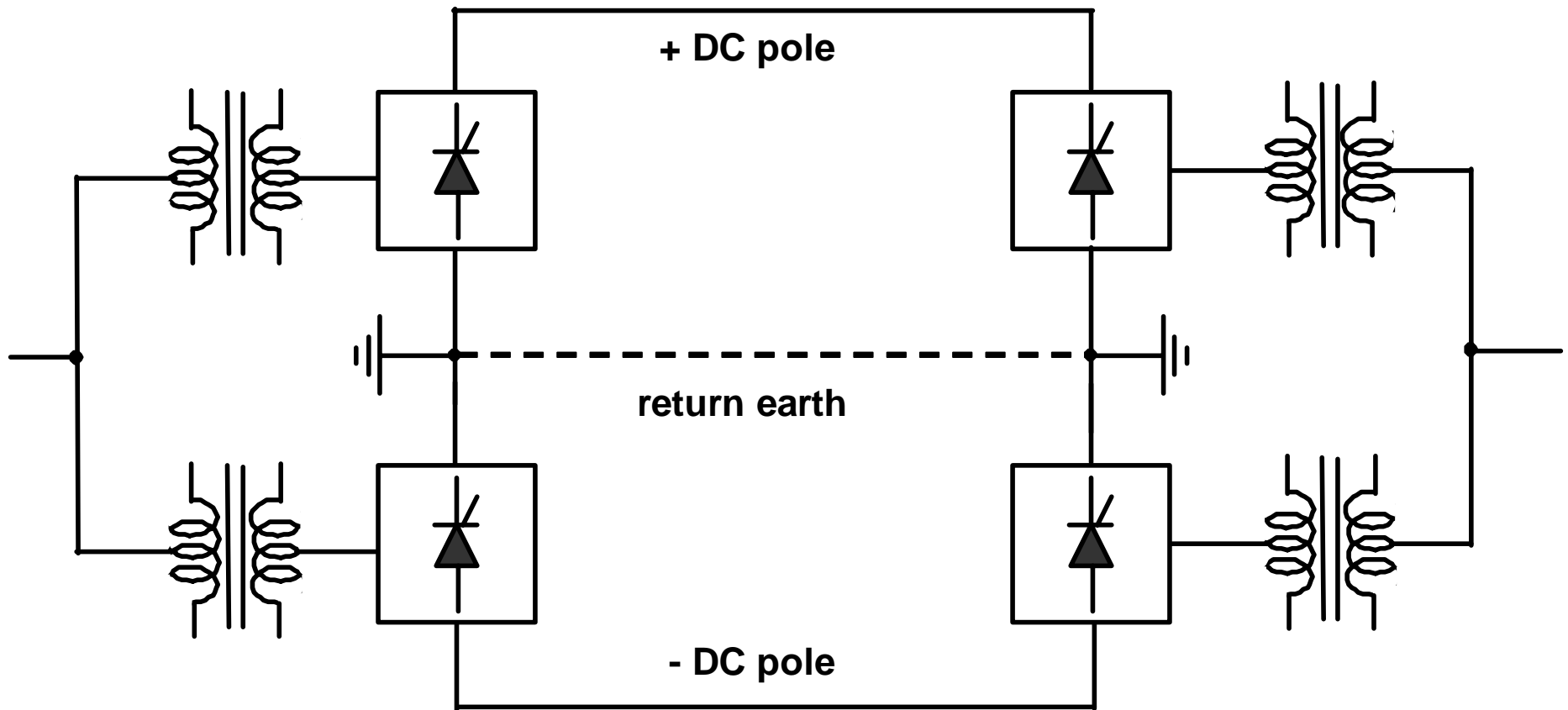2. Bipolar: There are two conductors (poles). One operates with positive polarity and the second with negative. During fault of one them, the bipolar acts as a monopolar



HVDC Light

1. HVDC Light unit sizes range from a few tens of MW to presently 350 MW and for DC voltages up to ± 150 kV and units can be connected in parallel.
2. HVDC Light consists of two elements: converter stations and a pair of cables. The converter stations are Voltage Source Converters (VSCs) employing Self-commutated switch

FACTS

1. POWER SYSTEMS
2. FACTS definition
3. FACTS controllers
4. Parallel controllers
5. Series controller
6. Series-parallel controllers
7. HVDC
8. Others

Battery Energy Storage System
Super conducting material